

Topics

- Single Cycle CPU Design (sections 4.1-4.4)

- **Pipelining**

- Overview (section 4.6)
- → Pipelined Datapath and control (section 4.7)
- Data hazard (section 4.8)
- Control hazard (section 4.9)


***Thus times do shift,
each thing his turn does hold;
New things succeed,
as former things grow old.***

Robert Herrick

Topics

- **Five functional units for pipelined datapath**
- **Graphically representing pipelines**
 - Single cycle
 - Multiple cycle
- **Control signals**


Review: Single-Cycle Datapath

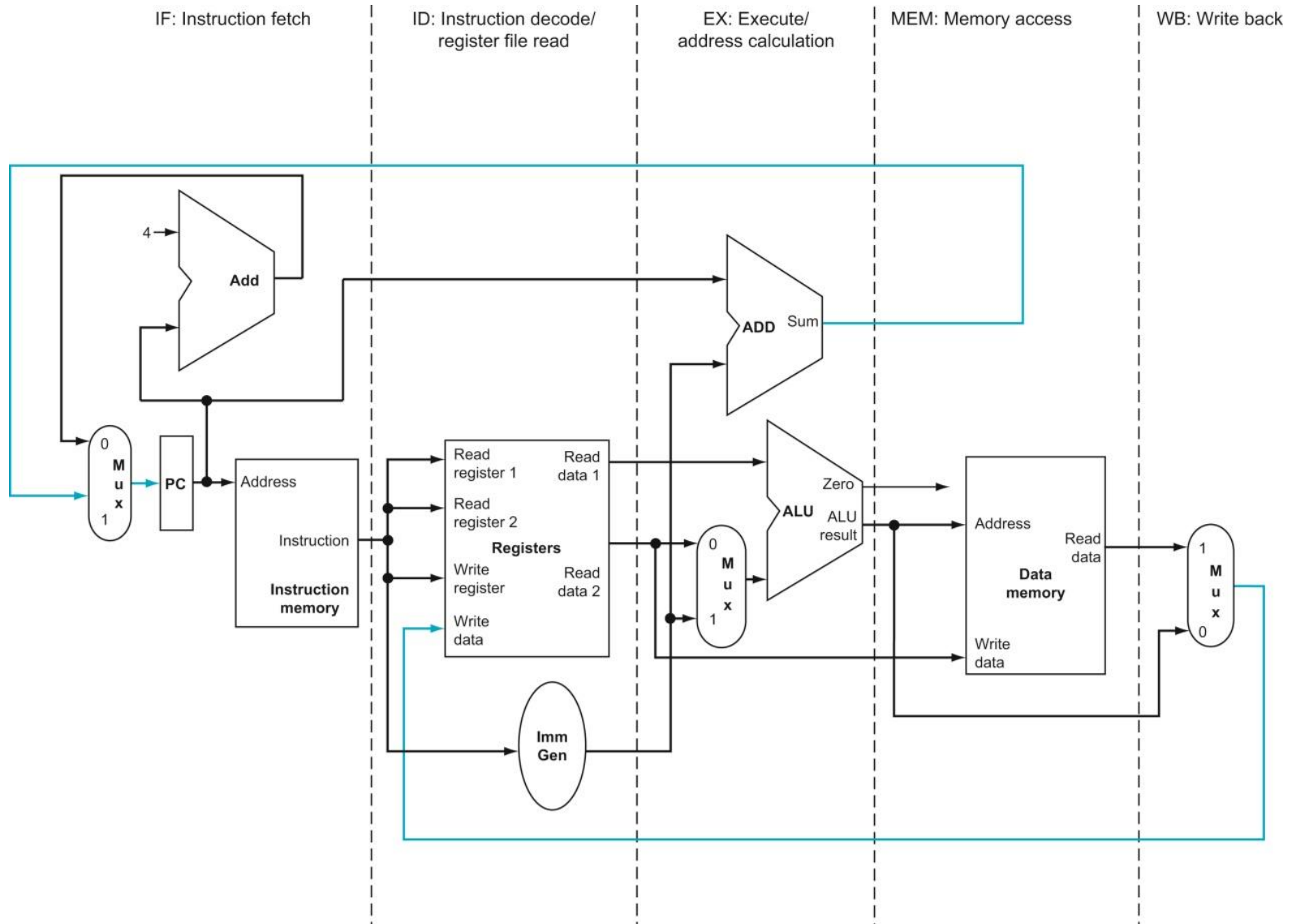

Observations


- **5-stage pipeline**
 - IF, ID, EX, MEM, WB
- **Left-to-right flow of instructions**
 - Instructions and data move generally from left to right
 - Two exceptions:
 - WB stage \Rightarrow data hazards
 - the selection of PC \Rightarrow control hazards
- **What to add to split the datapath into stages?**

Pipelined Datapath

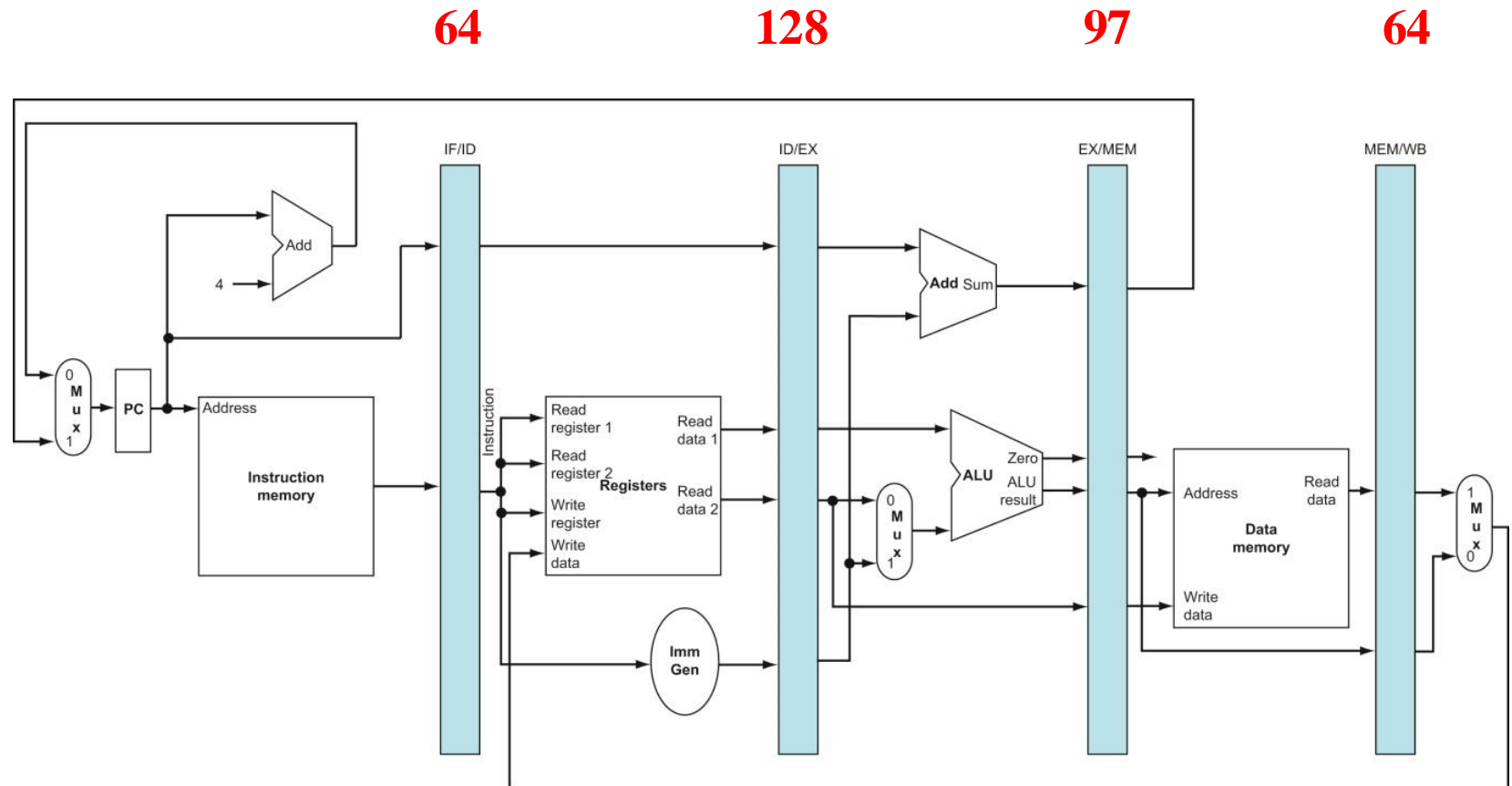


- **Add pipeline registers**
 - How many bits are stored in each pipeline register?
- **Why no pipeline register at the end of the WB stage?**

Pipelining the Load Instruction

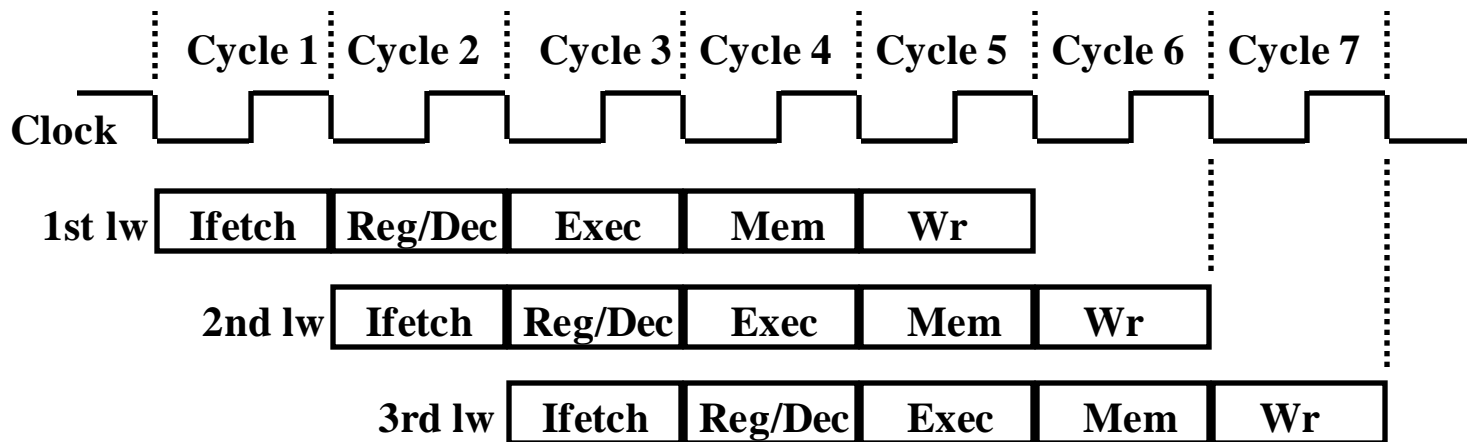


- The five independent functional units in the pipeline datapath are:
 - Instruction Memory for the **Ifetch** stage
 - Register File's Read ports (busA and busB) for the **Reg/Dec** stage
 - ALU for the **Exec** stage
 - Data Memory for the **Mem** stage
 - Register File's **Write** port (bus W) for the **Wr** stage
- **Effective (or average) number of cycles per instruction is ONE**

The Four Stages of Store

 


- **Ifetch: Instruction Fetch**
 - Fetch the instruction from the Instruction Memory
- **Reg/Dec: Registers Fetch and Instruction Decode**
- **Exec: Calculate the memory address**
- **Mem: Write the data into the Data Memory**


IF for Load, Store, ...

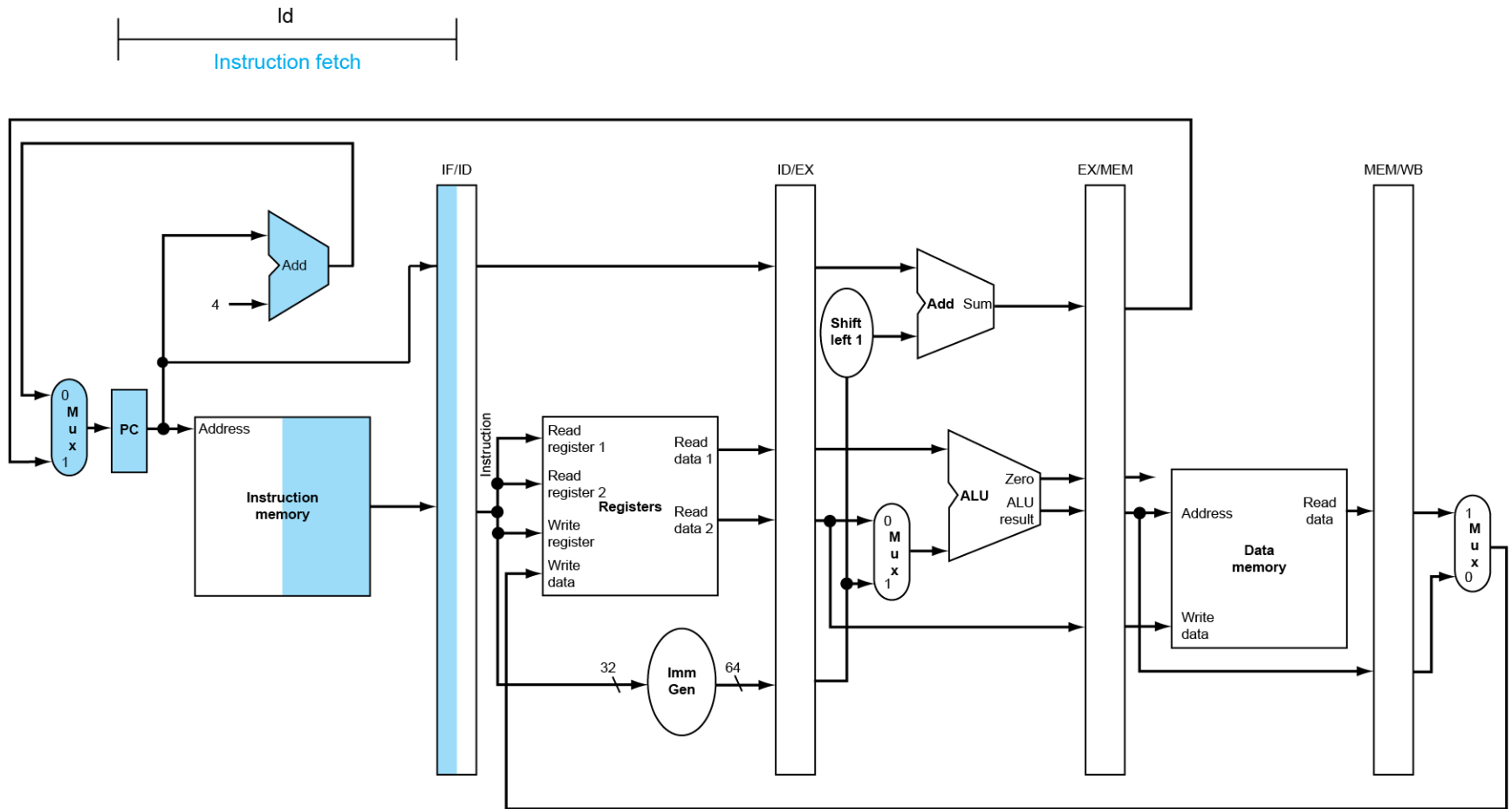


ID for Load, Store, ...

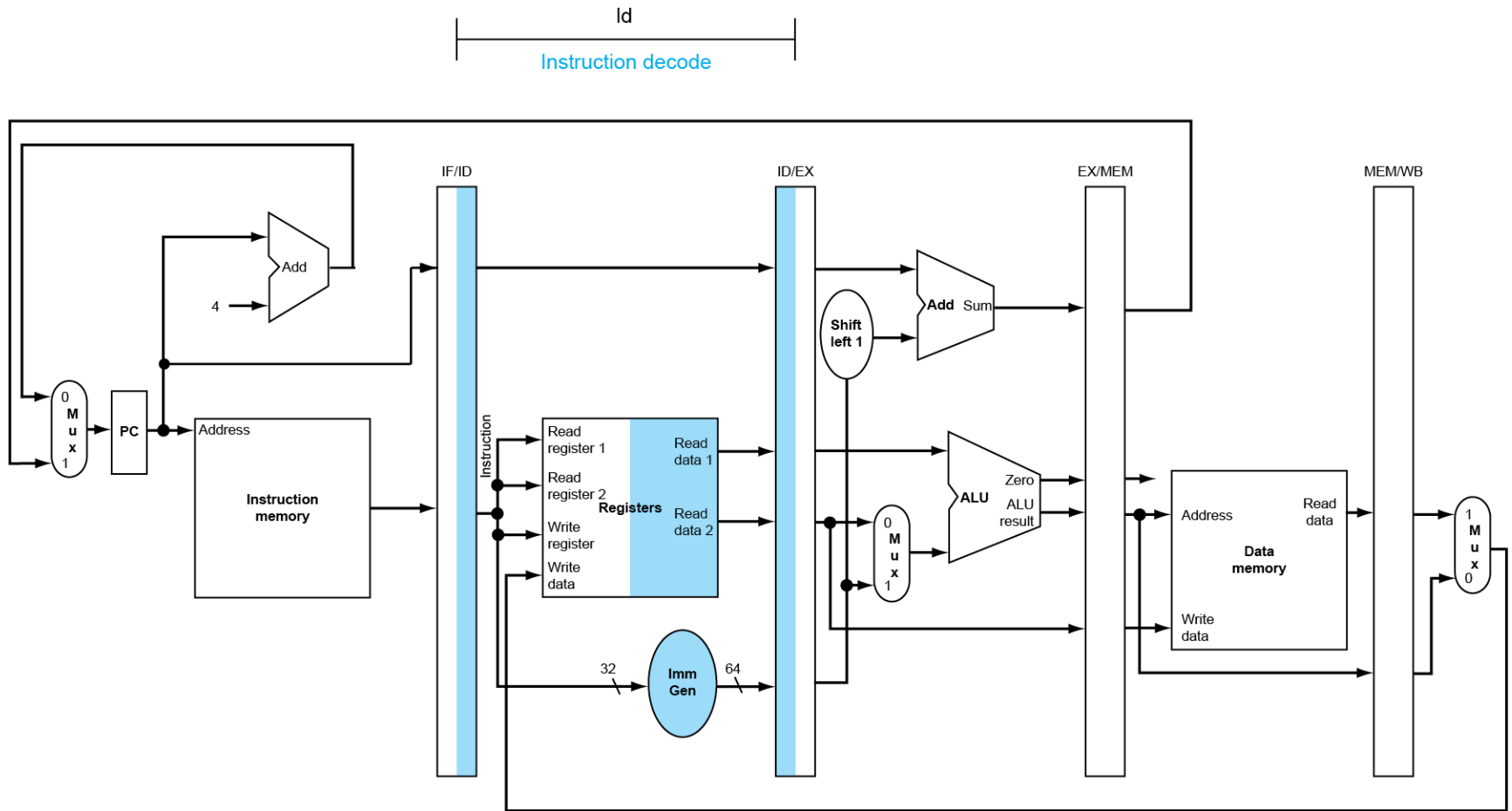


EX for Load

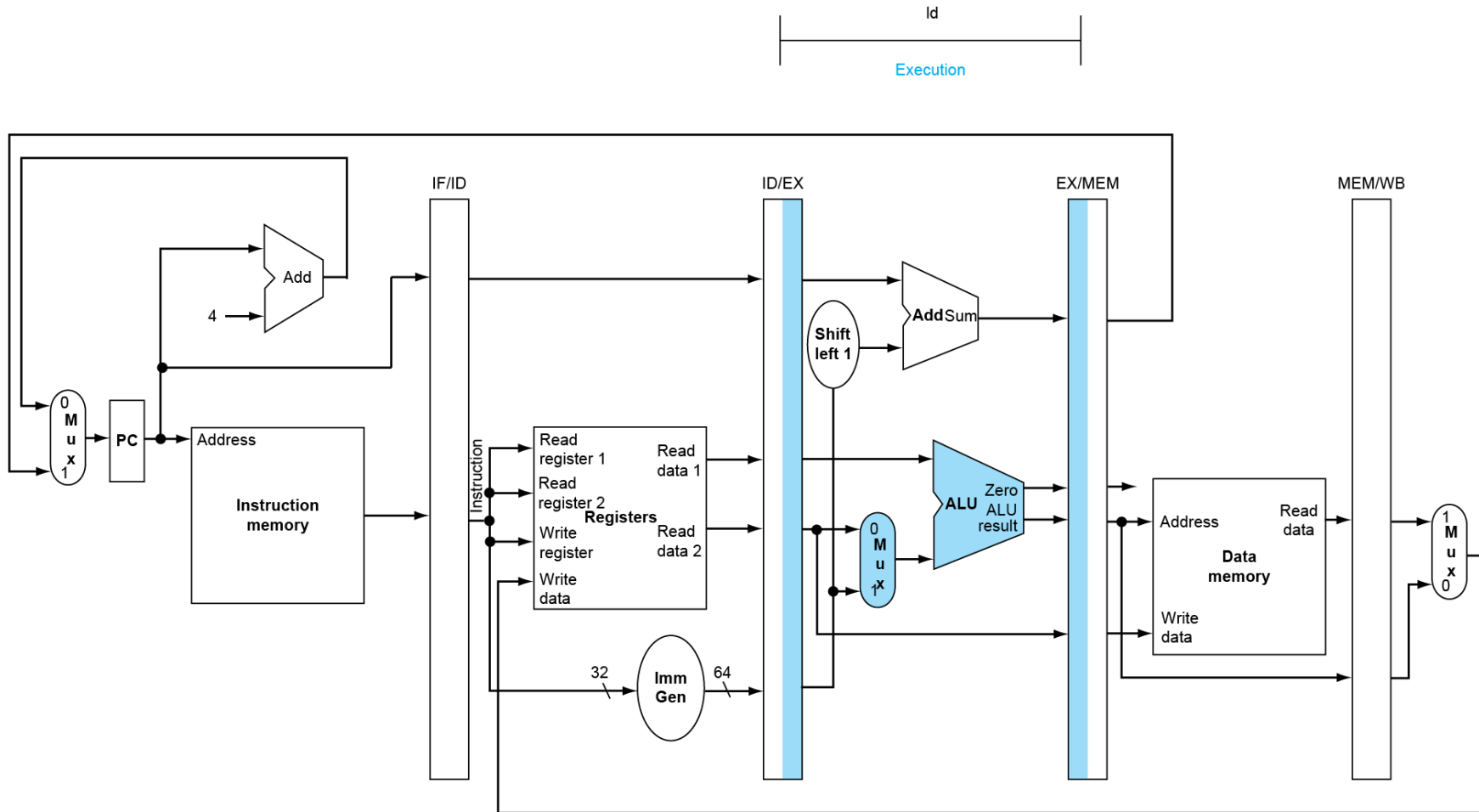


MEM for Load

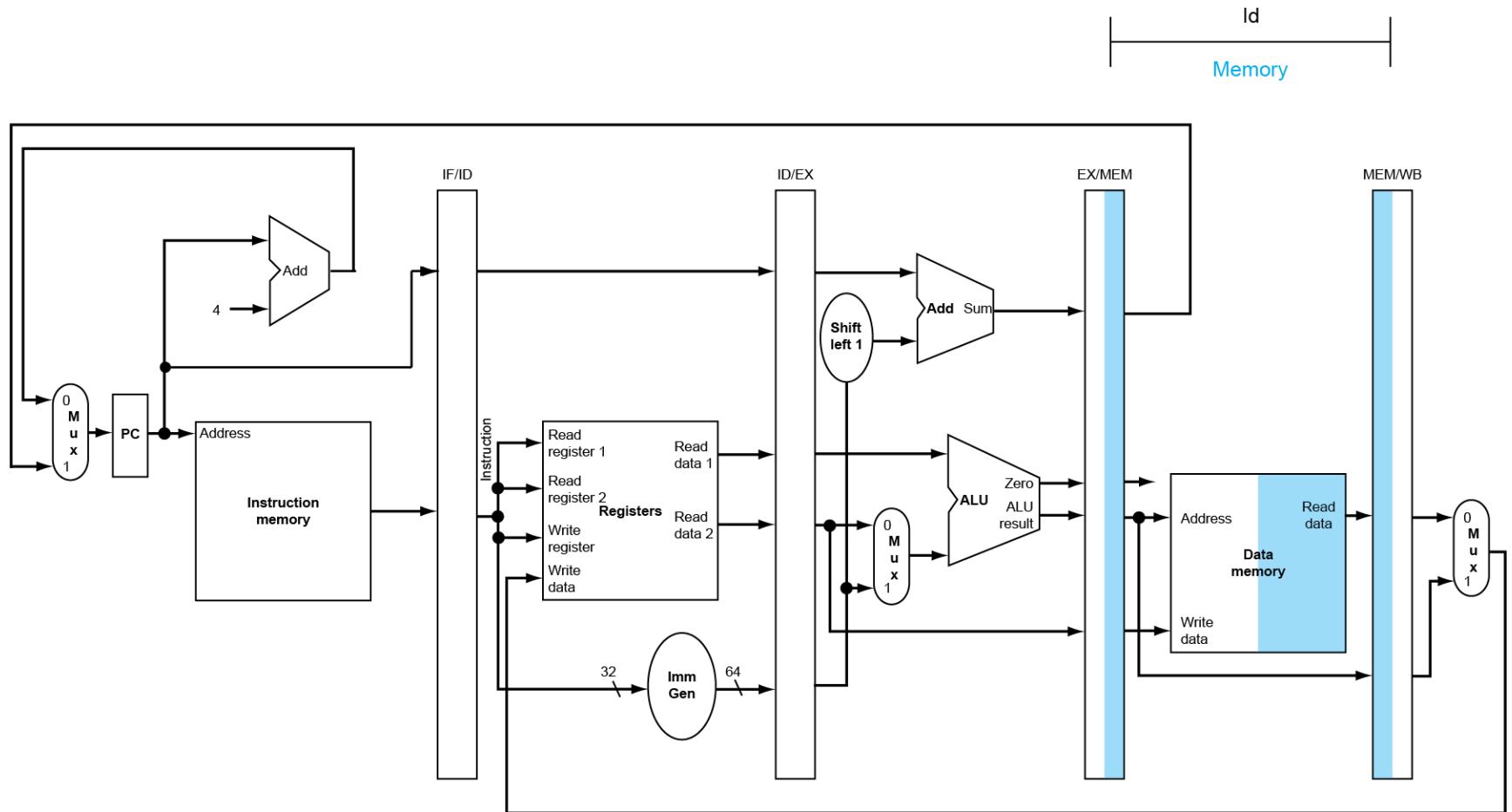

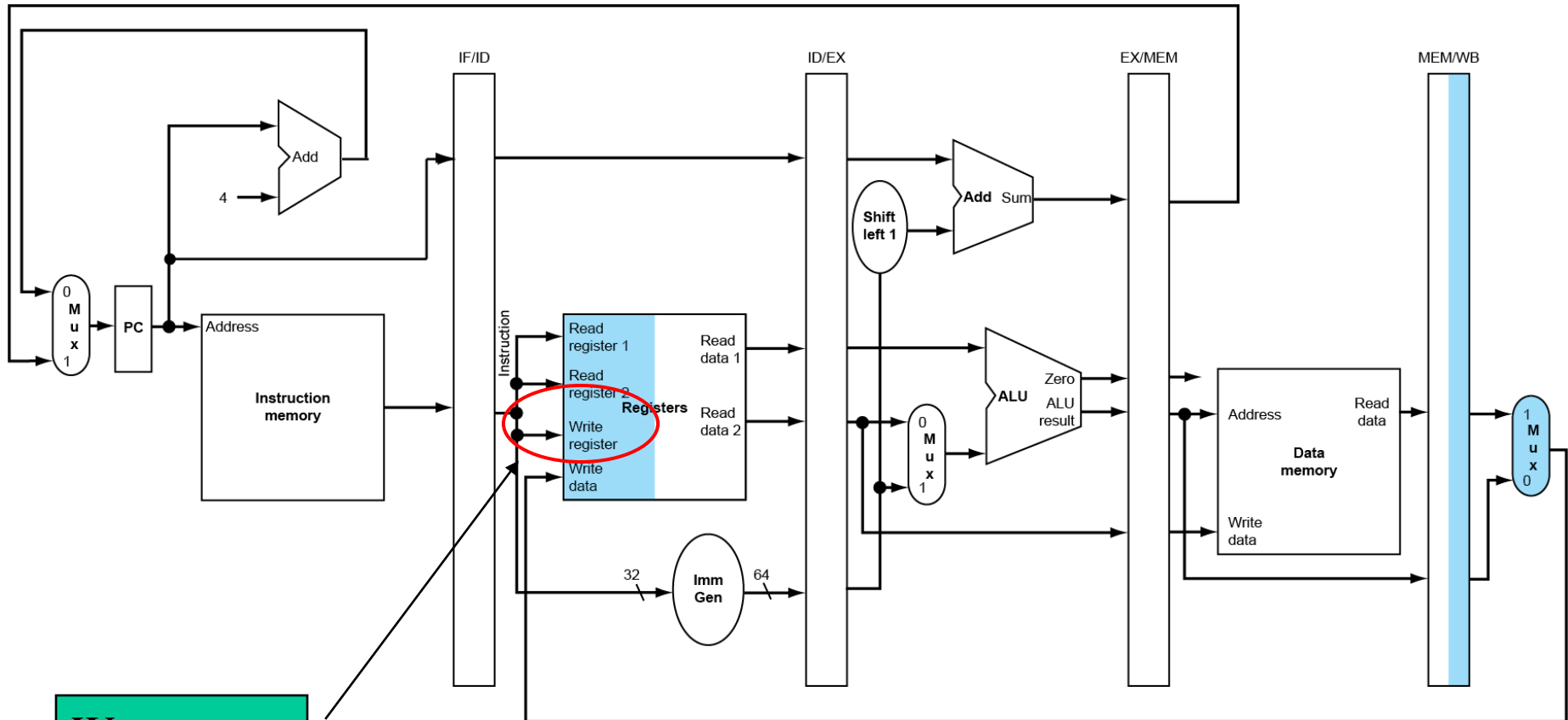


Wrong
register
number


Corrected Datapath for Load

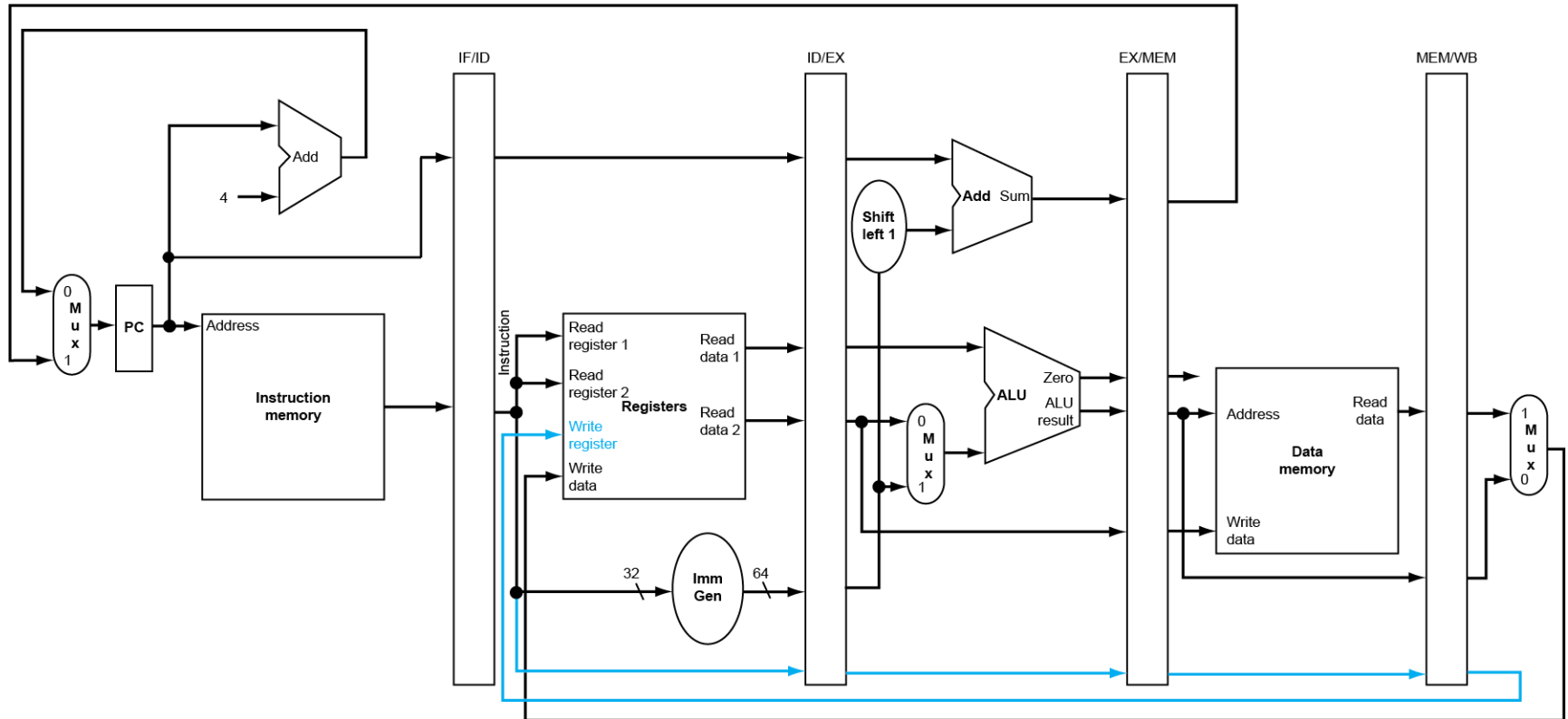


EX for Store

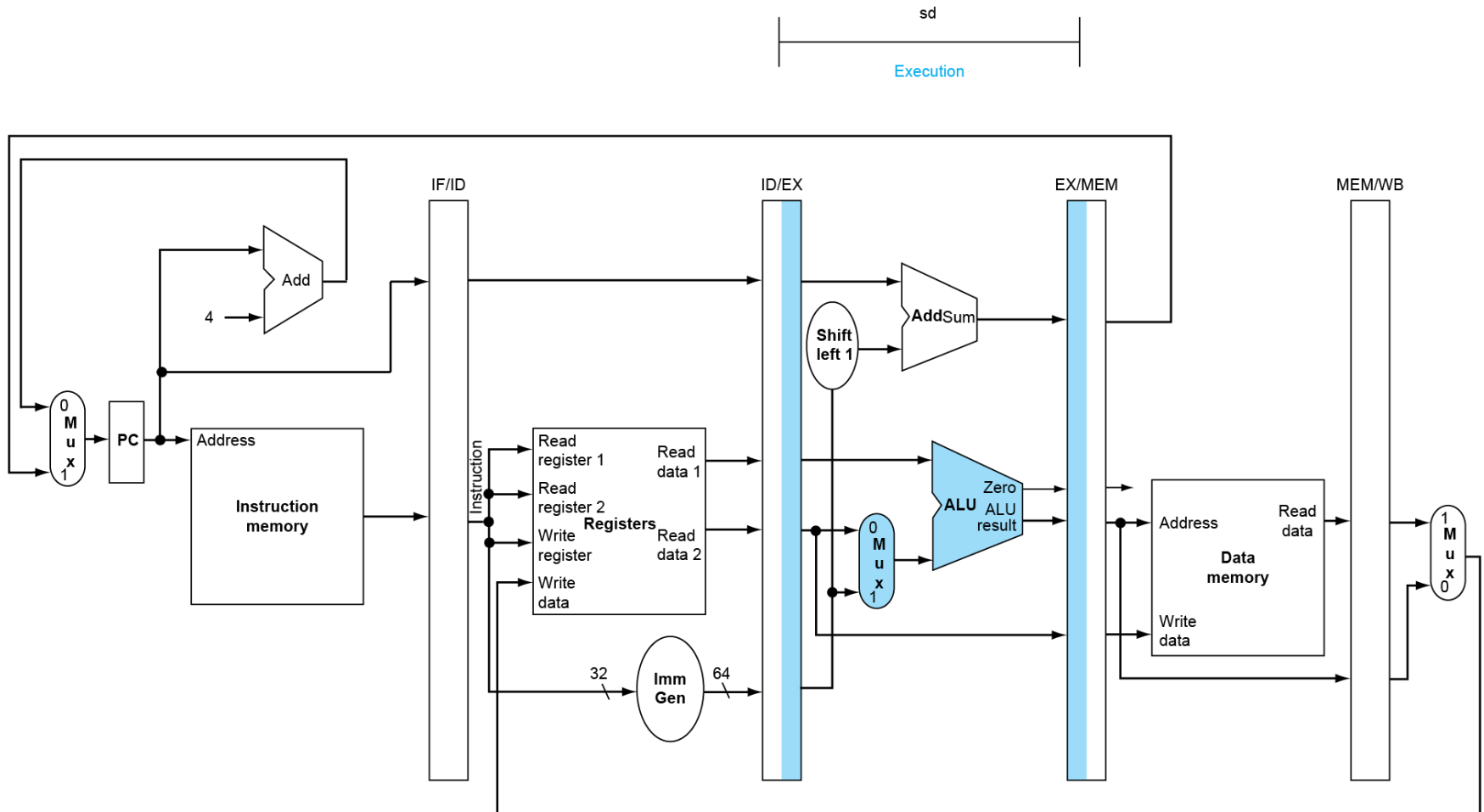

MEM for Store

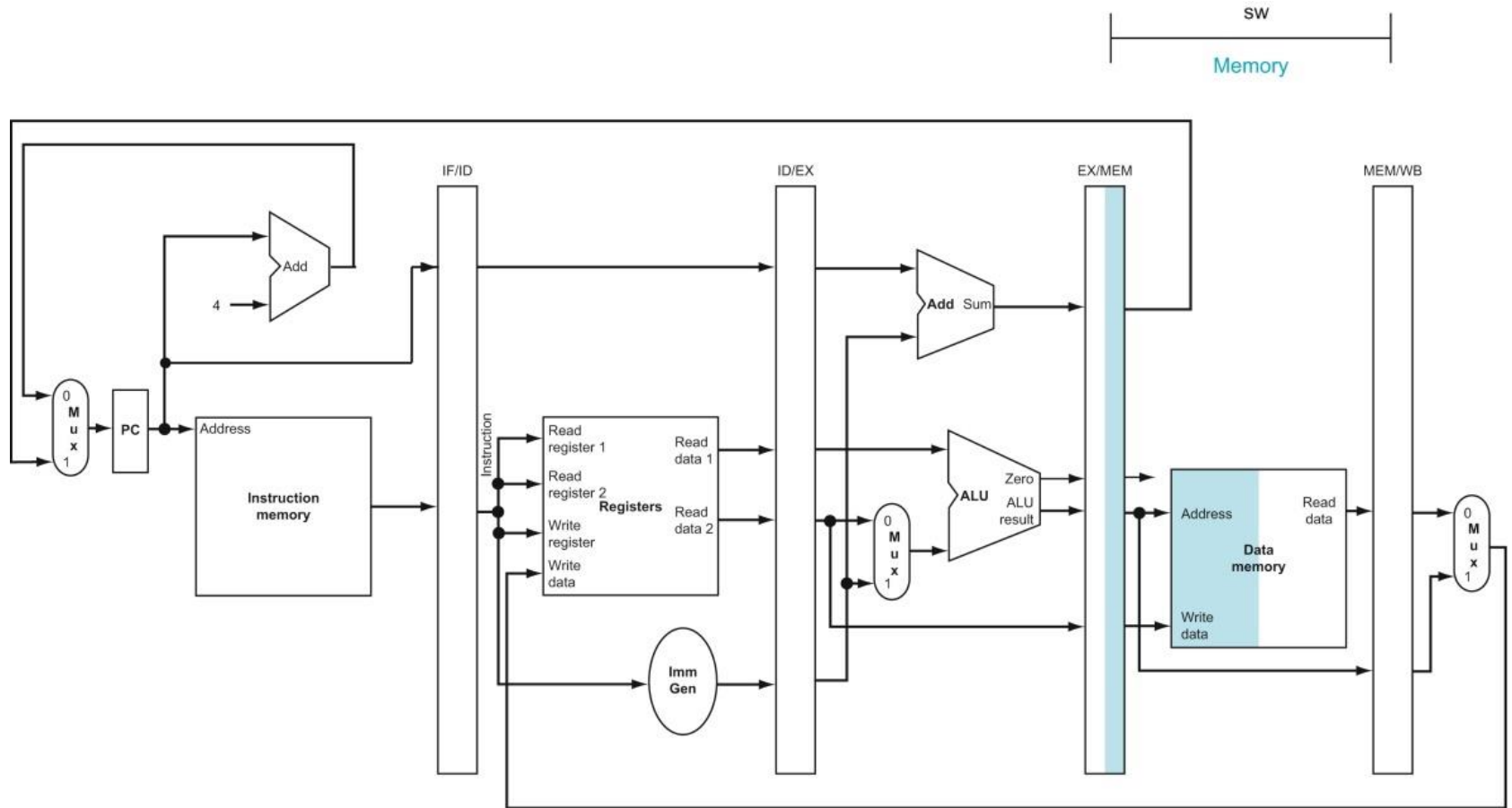


WB for Store

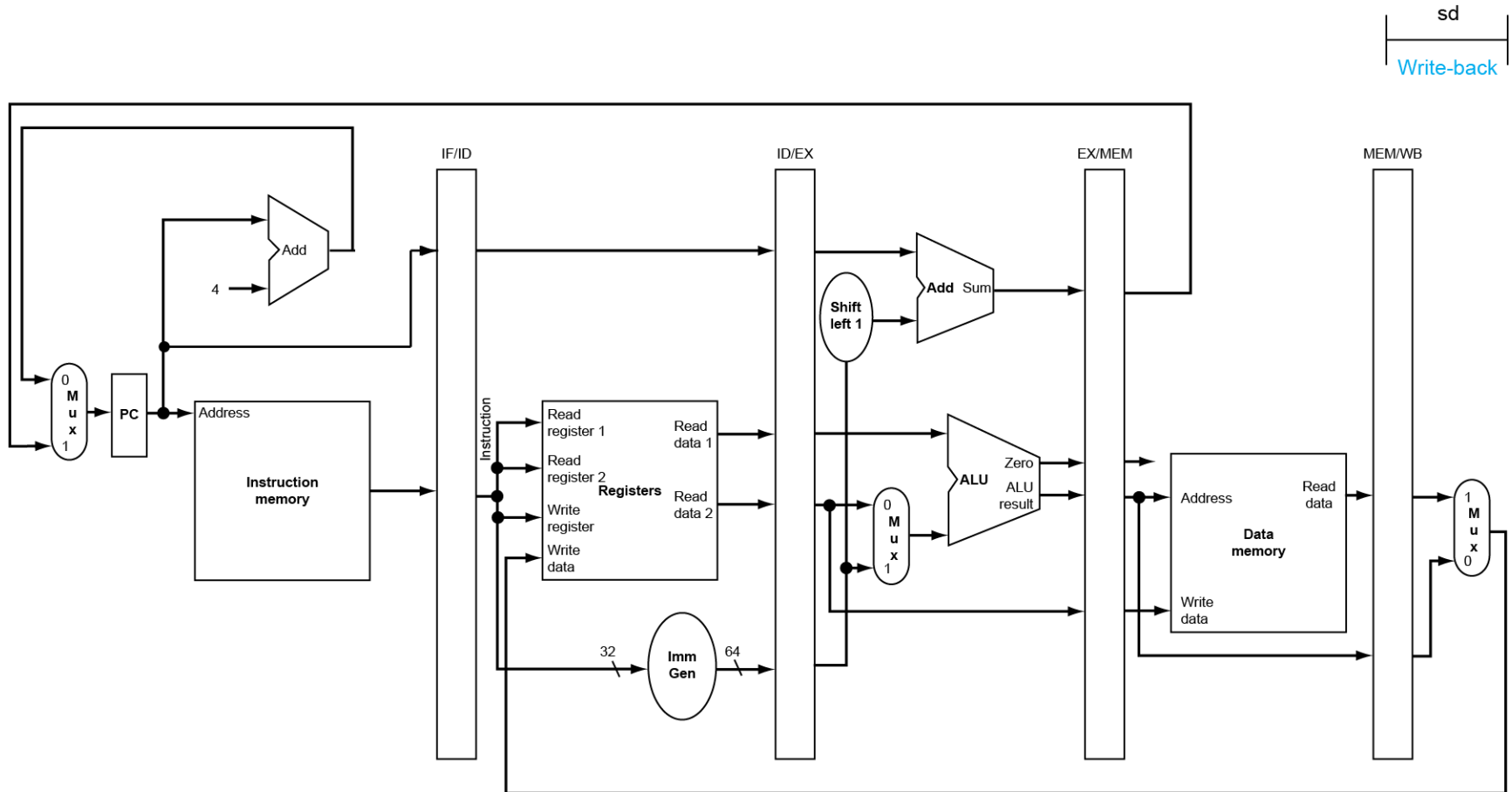

Observations from Load and Store

- **Pass information needed from an earlier stage to a later stage**
- **Each logical component of the datapath can be used only within a **single** pipeline stage**
 - functional units: IM, Reg read ports, ALU, DM, Reg write port
 - Otherwise, we would have structural hazard

The Four Stages of R-type

 

- **Ifetch: Instruction Fetch**

- Fetch the instruction from the Instruction Memory


- **Reg/Dec: Registers Fetch and Instruction Decode**

- **Exec:**

- ALU operates on the two register operands

- **Wr: Write the ALU output back to the register file**

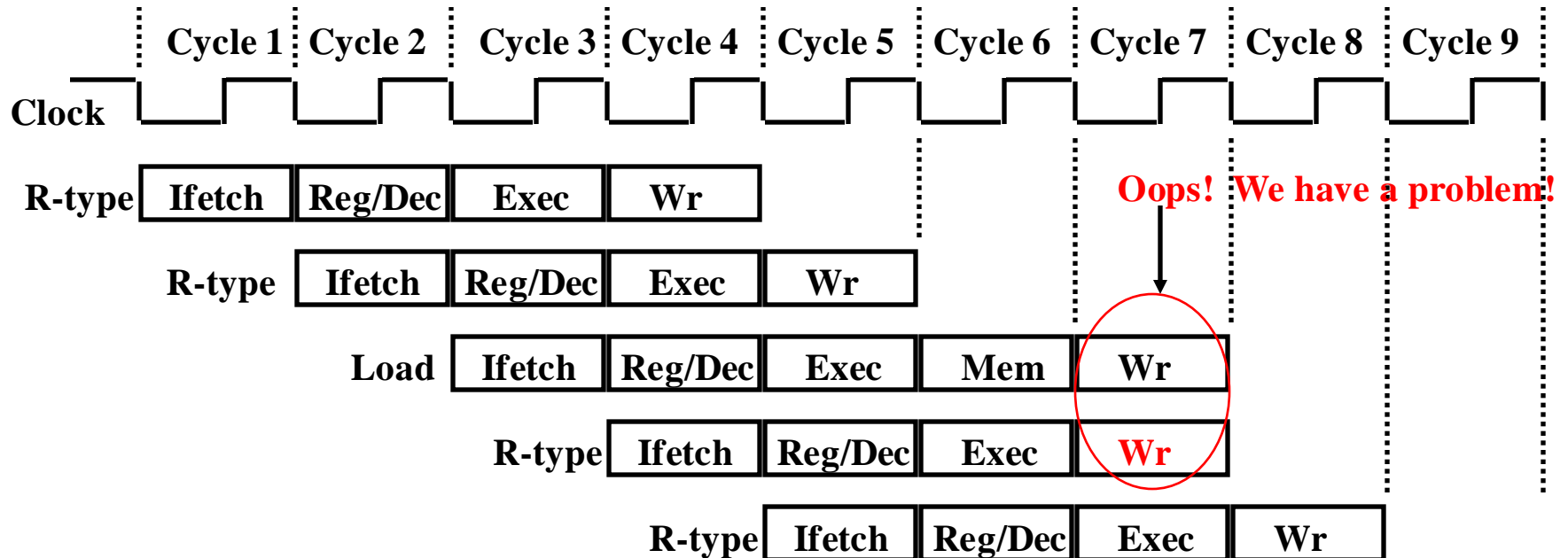Pipelining the R-type and Load Instructions




• We have pipeline conflict or structural hazard:


- Two instructions try to write to the register file at the same time!
- Only one write port

Important Observation

 - Each functional unit can only be used **once** per instruction
 - necessary condition for pipelining to work
- Each functional unit must be used at the **same** stage for all instructions:
 - Sufficient condition for pipelining to work
 - Load uses Register File's Write Port during its **5th** stage




 - R-type uses Register File's Write Port during its **4th** stage



- 2 Ways to resolve the pipeline hazard**

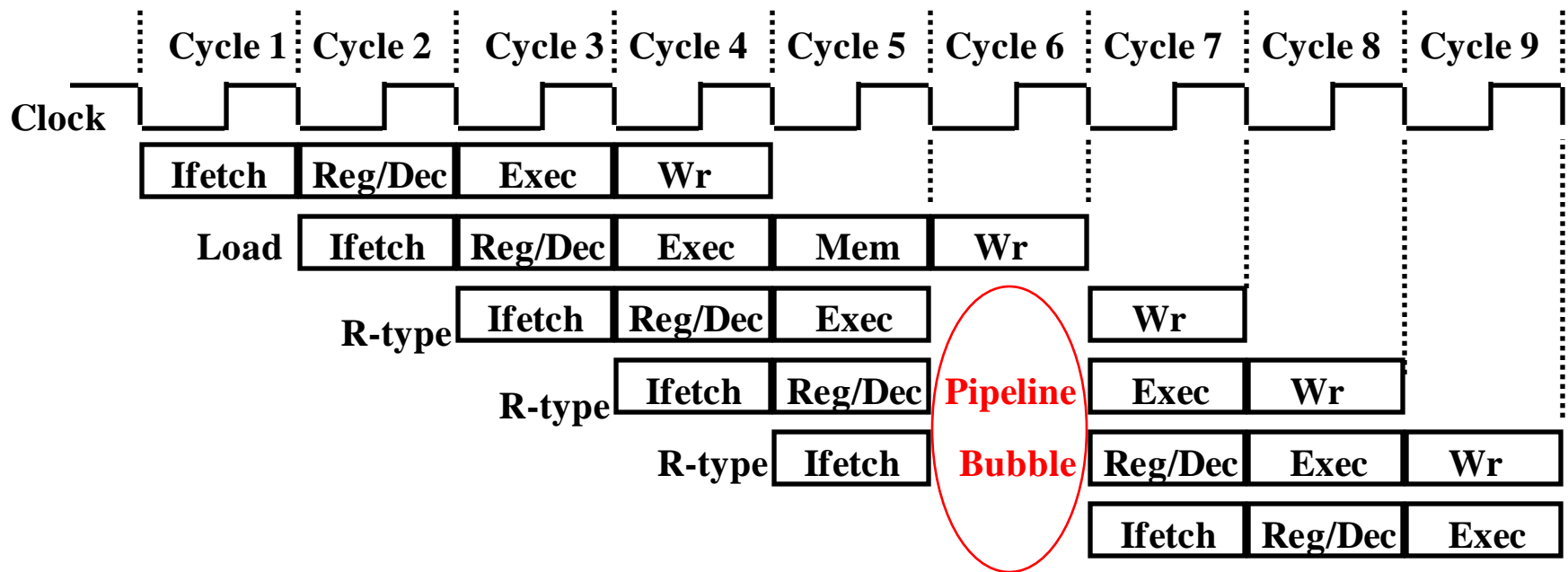
Solution 1: Insert “Bubble” into the Pipeline



Insert a “bubble” into the pipeline after lw to prevent 2 writes at the same cycle

- The control logic can be complex
- Lose instruction fetch and issue opportunity
- No instruction is started in Cycle 6!

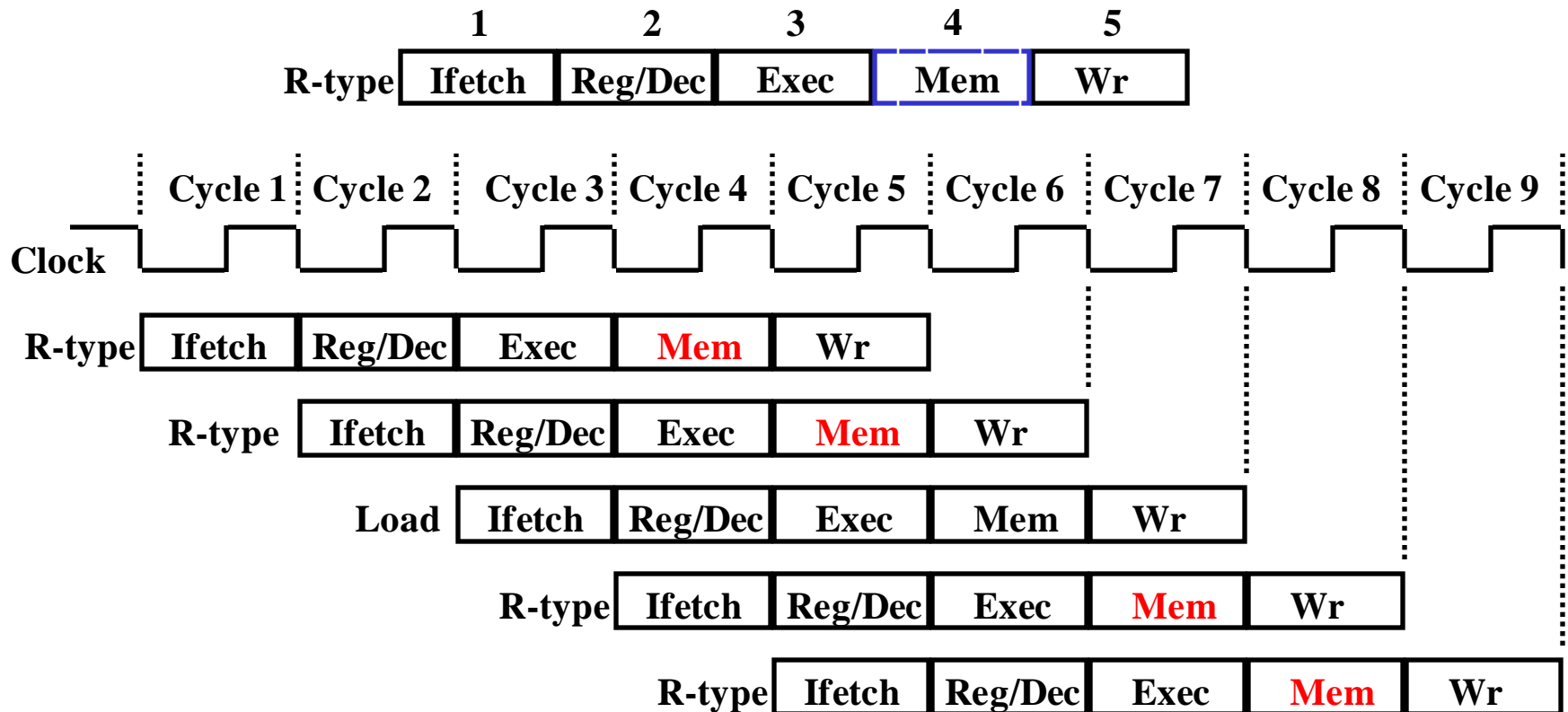
Solution 2: Delay R-type's Write by One Cycle



• Delay R-type's register write by one cycle:

- Now R-type instructions also use Reg File's write port at Stage 5
- Mem stage is a **NOOP** stage: nothing is being done

The Four Stages of Beq

 

- **Ifetch: Instruction Fetch**

- Fetch the instruction from the Instruction Memory

- **Reg/Dec:**

- Registers Fetch and Instruction Decode


- **Exec:**

- compares the two register operand,
- calculate branch target address

- **MEM**

- Use the Zero result to decide which adder result to store into PC

Multiple-clock-cycle Pipeline Diagram

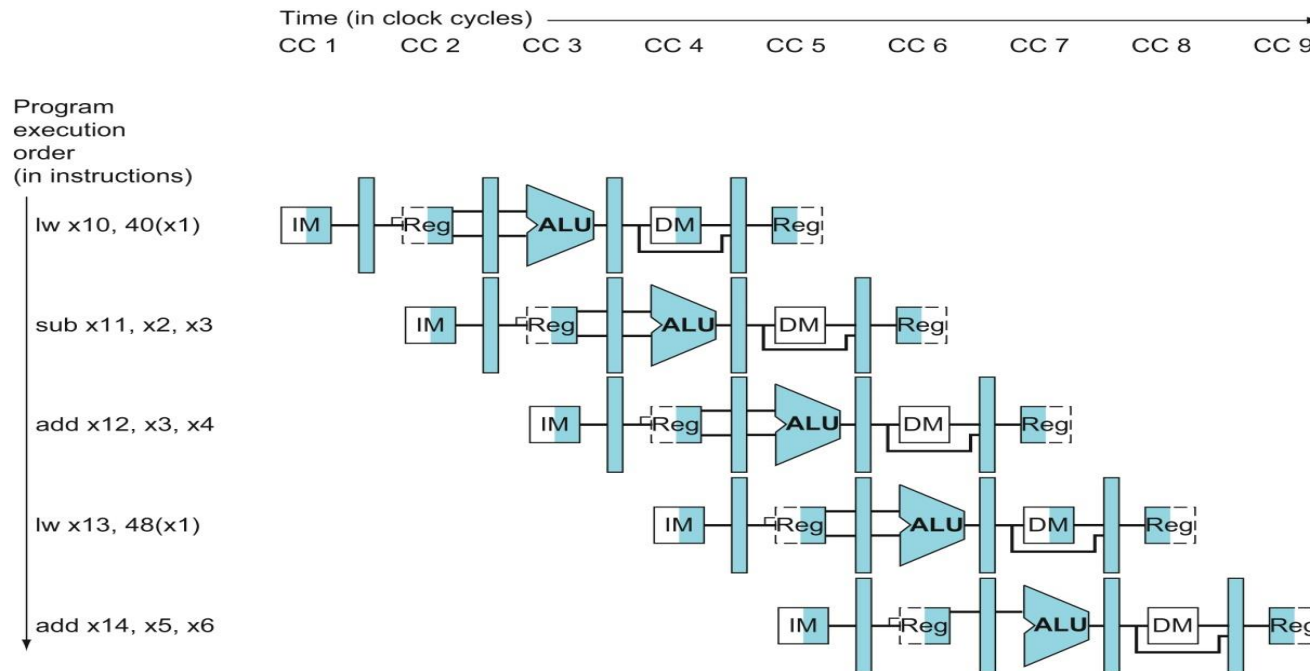

- Can help with answering questions like:
 - how many cycles does it take to execute this code?
 - what is the ALU doing during cycle 4?

Single Clock Cycle Pipeline Diagram

State of pipeline in a given cycle (cycle 5)

