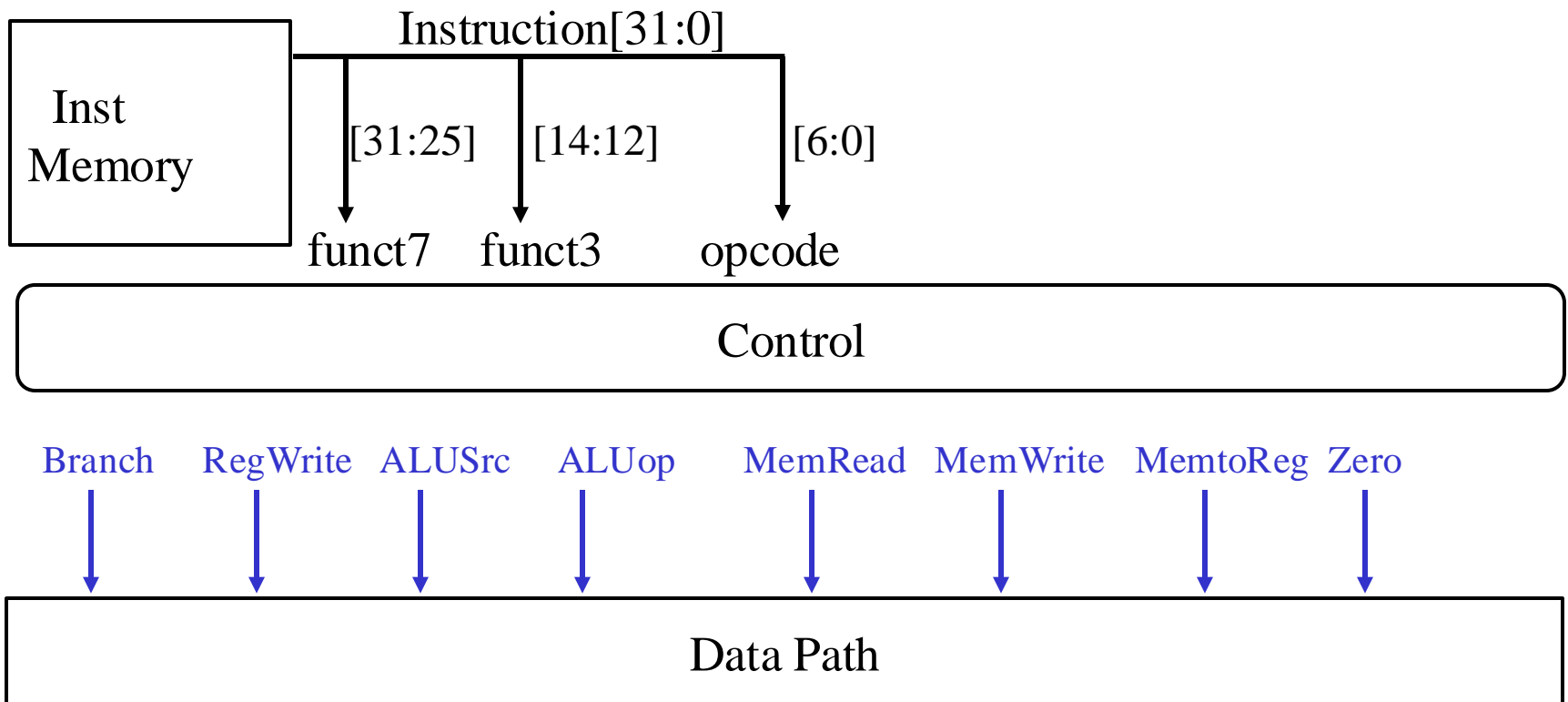


# ***How to Design a Processor: Step by Step***

1. Analyze instruction set => datapath requirements
  1. the meaning of each instruction is given by the *register transfers*
  2. datapath must include storage element for registers
  3. datapath must support each register transfer
2. Select the set of datapath components and establish clocking methodology
3. Assemble the datapath meeting the requirements
4. **Analyze the implementation of each instruction to determine the settings of the control points that affects the register transfer**
5. Assemble the control logic

# Step 4: Given Datapath: RTL → Control

31	27	26	25	24	20	19	15	14	12	11	7	6	0	
funct7				rs2		rs1		funct3		rd		opcode		R-type
imm[11:0]						rs1		funct3		rd		opcode		I-type
imm[11:5]				rs2		rs1		funct3		imm[4:0]		opcode		S-type
imm[12:10:5]				rs2		rs1		funct3		imm[4:1:11]		opcode		B-type




# Main Control Unit

- › Generate control signals for datapath elements & 2 bits for ALUop
- › Control signals derived from instruction


R-type	<table><tr><td>funct7</td><td>rs2</td><td>rs1</td><td>funct3</td><td>rd</td><td>opcode</td></tr><tr><td>7 bits</td><td>5 bits</td><td>5 bits</td><td>3 bits</td><td>5 bits</td><td>7 bits</td></tr></table>	funct7	rs2	rs1	funct3	rd	opcode	7 bits	5 bits	5 bits	3 bits	5 bits	7 bits
funct7	rs2	rs1	funct3	rd	opcode								
7 bits	5 bits	5 bits	3 bits	5 bits	7 bits								
Store	<table><tr><td>immediate[1:5]bits</td><td>rs2</td><td>rs1</td><td>funct3</td><td>immediate[4:0] 5 bits</td><td>opcode</td></tr><tr><td></td><td>5 bits</td><td>5 bits</td><td>3 bits</td><td></td><td>7 bits</td></tr></table>	immediate[1:5]bits	rs2	rs1	funct3	immediate[4:0] 5 bits	opcode		5 bits	5 bits	3 bits		7 bits
immediate[1:5]bits	rs2	rs1	funct3	immediate[4:0] 5 bits	opcode								
	5 bits	5 bits	3 bits		7 bits								
Load	<table><tr><td colspan="2">immediate</td><td>rs1</td><td>funct3</td><td>rd</td><td>opcode</td></tr><tr><td colspan="2"></td><td></td><td></td><td></td><td></td></tr></table>	immediate		rs1	funct3	rd	opcode						
immediate		rs1	funct3	rd	opcode								
Branch	<table><tr><td>imm[12 10:5]</td><td>rs2</td><td>rs1</td><td>funct3</td><td>imm[4:1 11]</td><td>opcode</td></tr><tr><td>7 bits</td><td>5 bits</td><td>5 bits</td><td>3 bits</td><td>5 bits</td><td>7 bits</td></tr></table>	imm[12 10:5]	rs2	rs1	funct3	imm[4:1 11]	opcode	7 bits	5 bits	5 bits	3 bits	5 bits	7 bits
imm[12 10:5]	rs2	rs1	funct3	imm[4:1 11]	opcode								
7 bits	5 bits	5 bits	3 bits	5 bits	7 bits								


# Main Control Unit

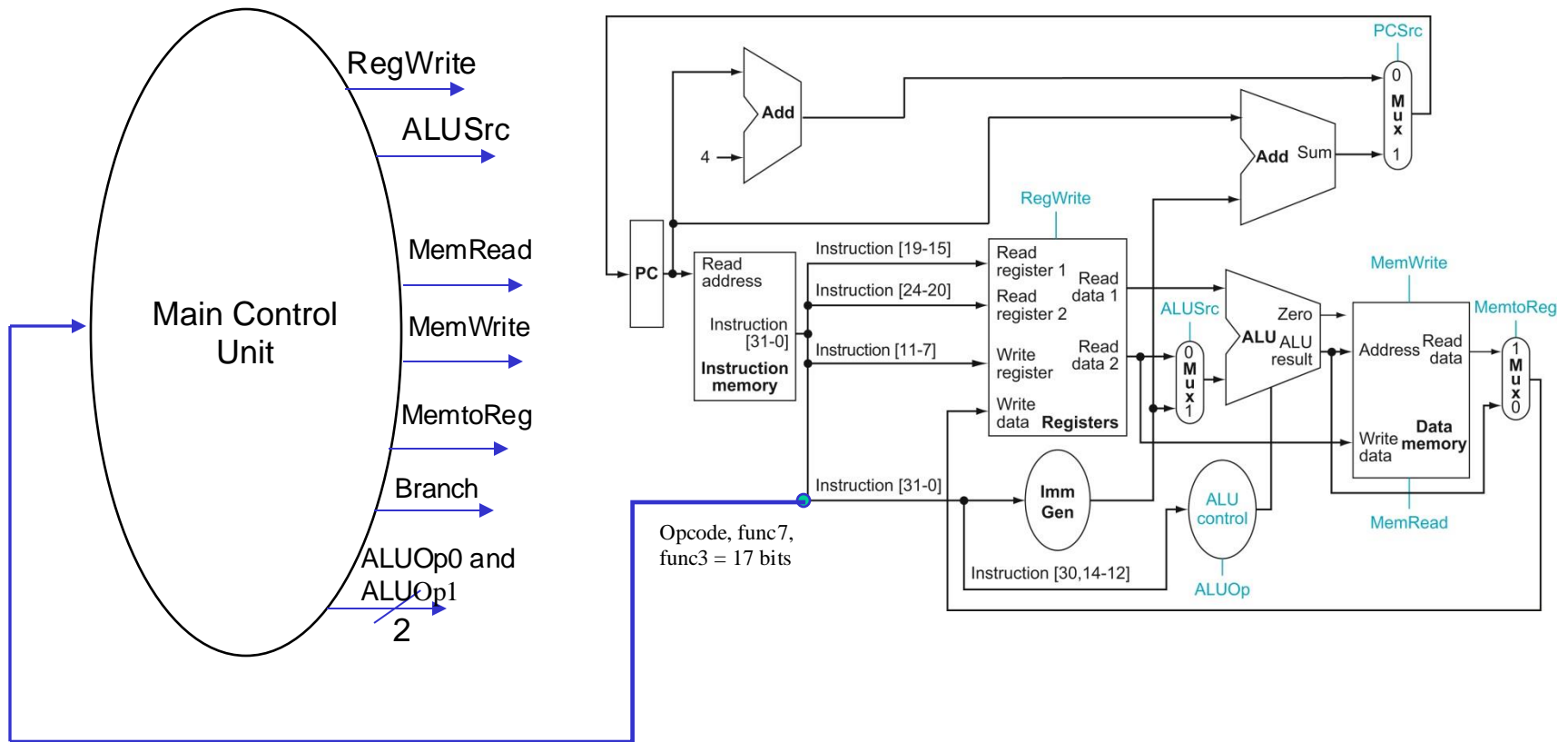

# *Branch is Special*

- › control alone is not enough

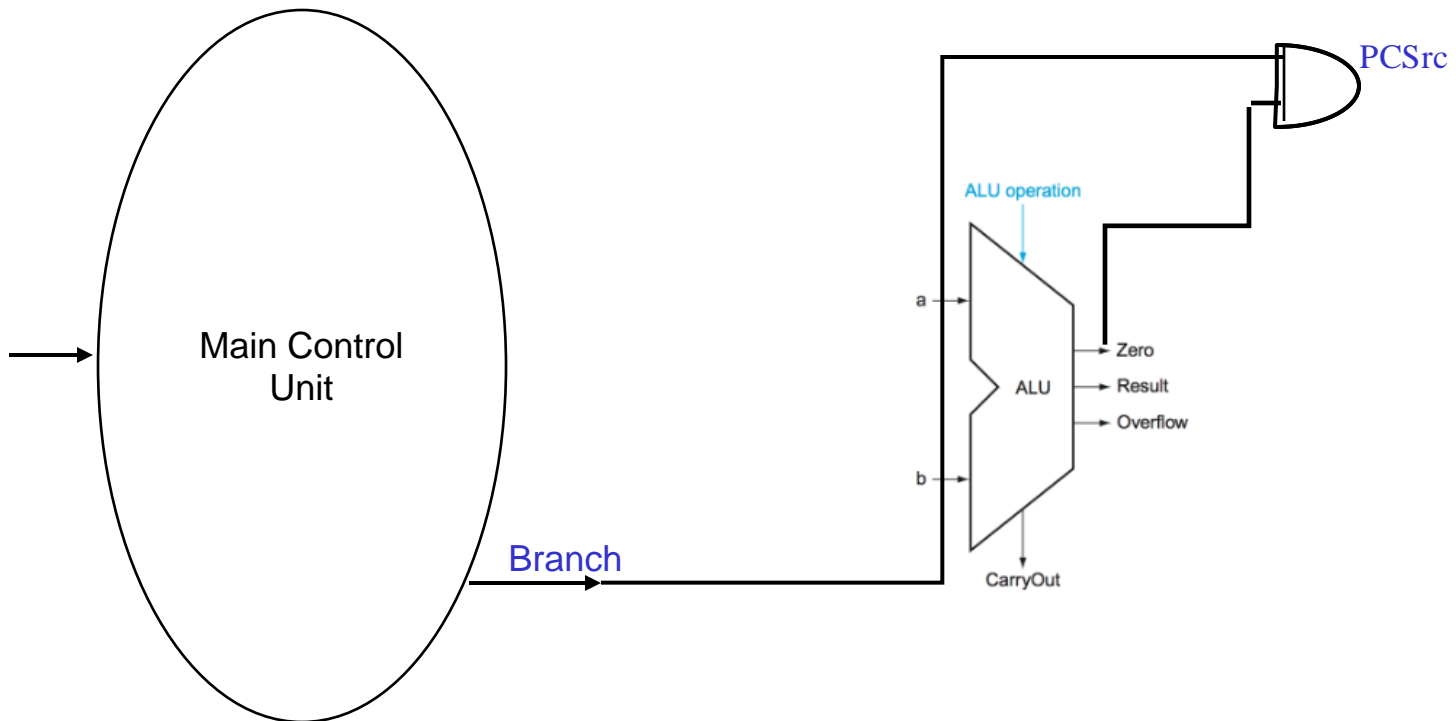

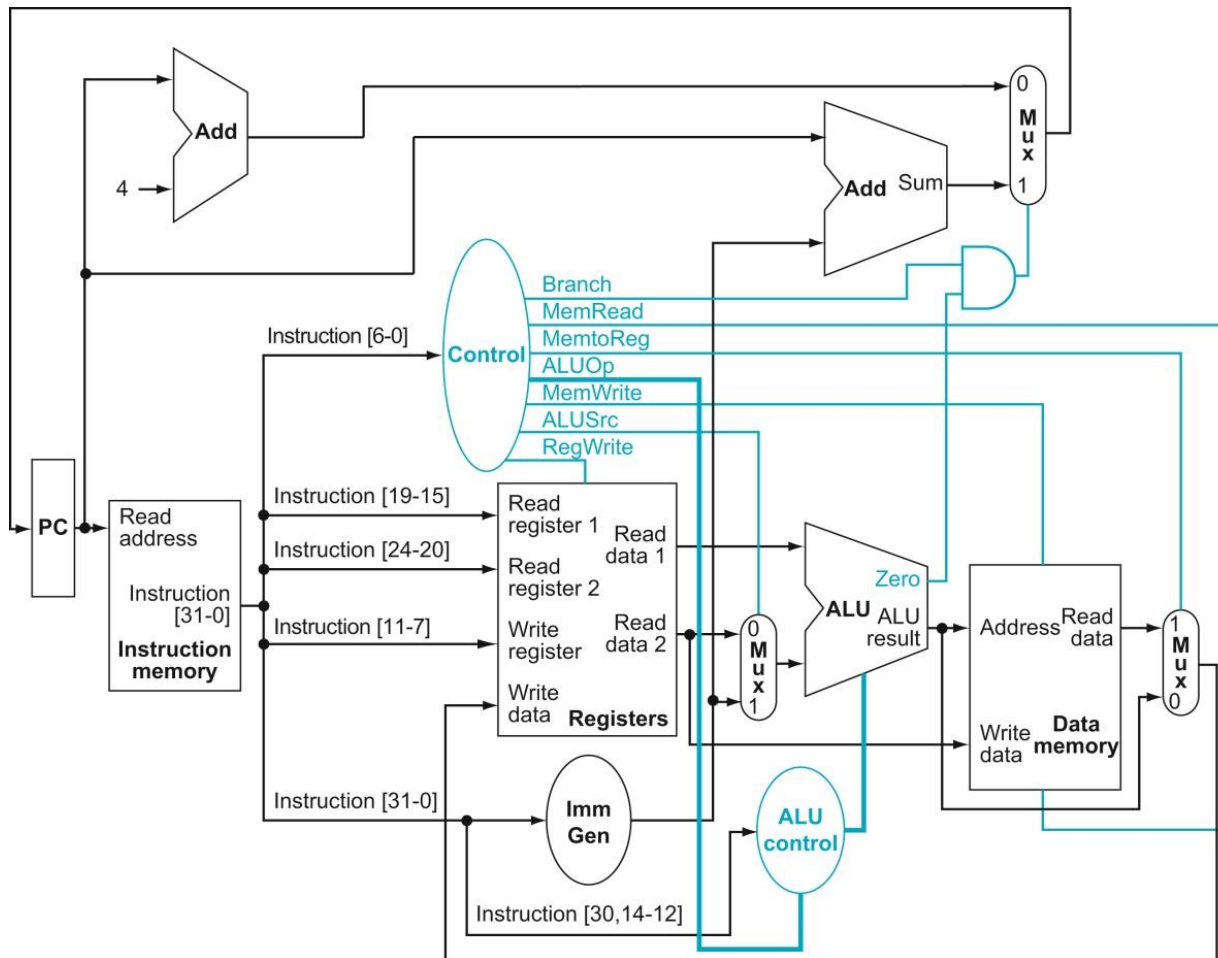

# Control

---

- Controlling the flow of data (multiplexor inputs)
  - Design the Main Control Unit
- Selecting the operations to perform (ALU, read/write, etc.)
  - Design the ALU Control Unit
- Information comes from the 32 bits of the instruction
- Example: add t0, s1, s2

## Instruction Format

funct7	rs2	rs1	funct3	rd	opcode
0000000	01010	01001	000	00101	0110011

- ALU's operation based on instruction type and function code

# ***Design of the Main Control Unit***

---

## ● **Seven control signals**

- RegWrite
- ALUSrc
- PCSrc
- MemRead
- MemWrite
- MemtoReg
  
- ALUOp
  - 00: loads and stores
  - 01: beq
  - 10: R-type, determined by func7 and func3



# ***How to Design a Processor: Step by Step***


1. Analyze instruction set => datapath requirements
  1. the meaning of each instruction is given by the *register transfers*
  2. datapath must include storage element for registers
  3. datapath must support each register transfer
2. Select the set of datapath components and establish clocking methodology
3. Assemble the datapath meeting the requirements
4. Analyze the implementation of each instruction to determine the settings of the control points that affects the register transfer
5. **Assemble the control logic**

# Control Signals

---


1	RegWrite = 1	The register on the Write register input is written with the data on the Write data input (at the next clock edge)
2	ALUSrc = 0	The second ALU operand comes from Read data 2
	ALUSrc = 1	The second ALU operand comes from the sign-extension unit
3	PCSrc = 0	The PC is replaced with PC+4
	PCSrc = 1	The PC is replaced with the branch target address
4	MemtoReg = 0	The value input to the regular write data input comes from the ALU
	MemtoReg = 1	The value input to the regular write data input comes from the data memory
5	MemRead = 1	Read data memory
6	MemWrite = 1	Write data memory

# Control for R-Format Instructions

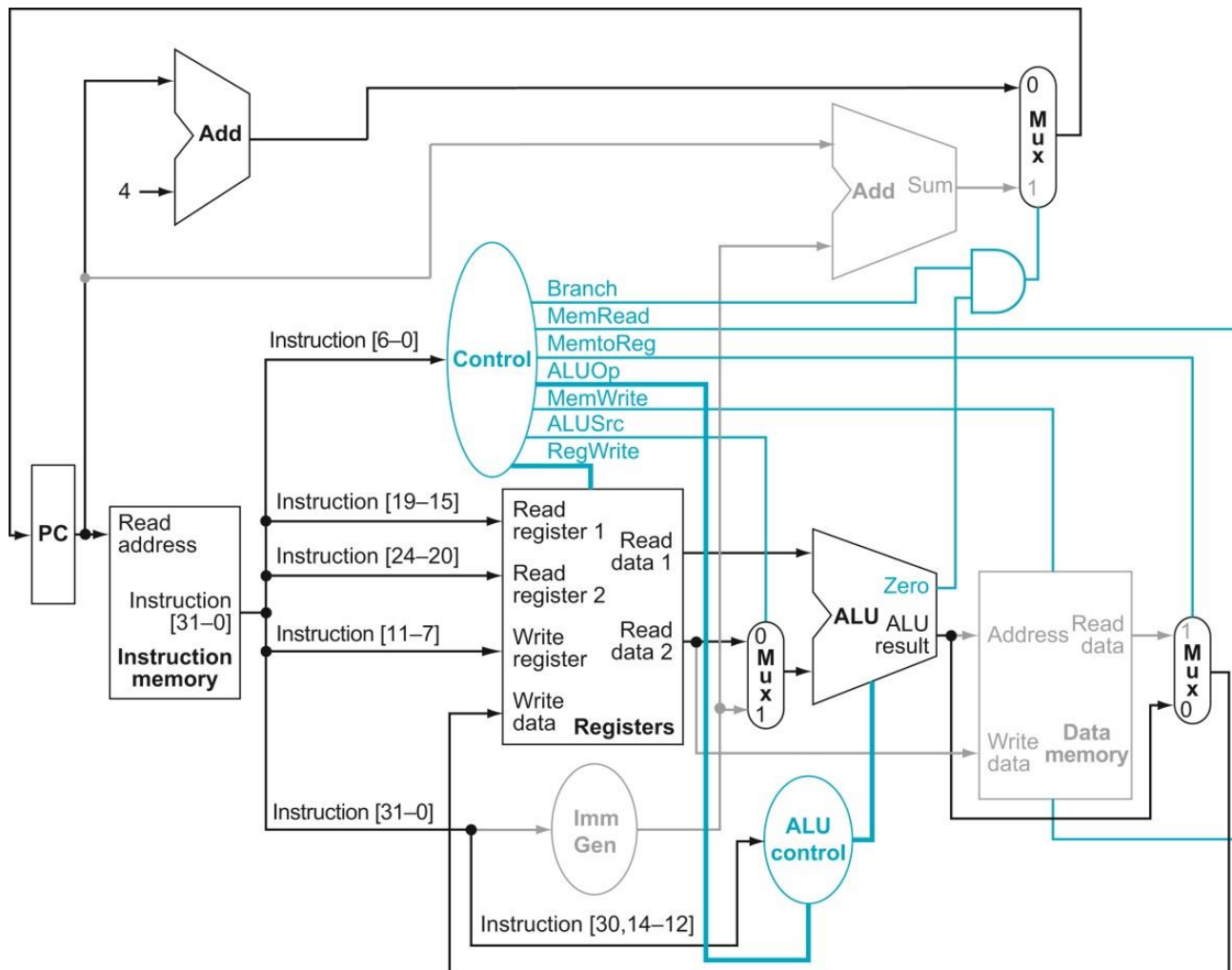


RegWrite	1
ALUSrc	0
Branch	0
MemtoReg	0
MemRead	0
MemWrite	0
ALUOp1	1
ALUOp0	0

# Control for Load/Store Instructions

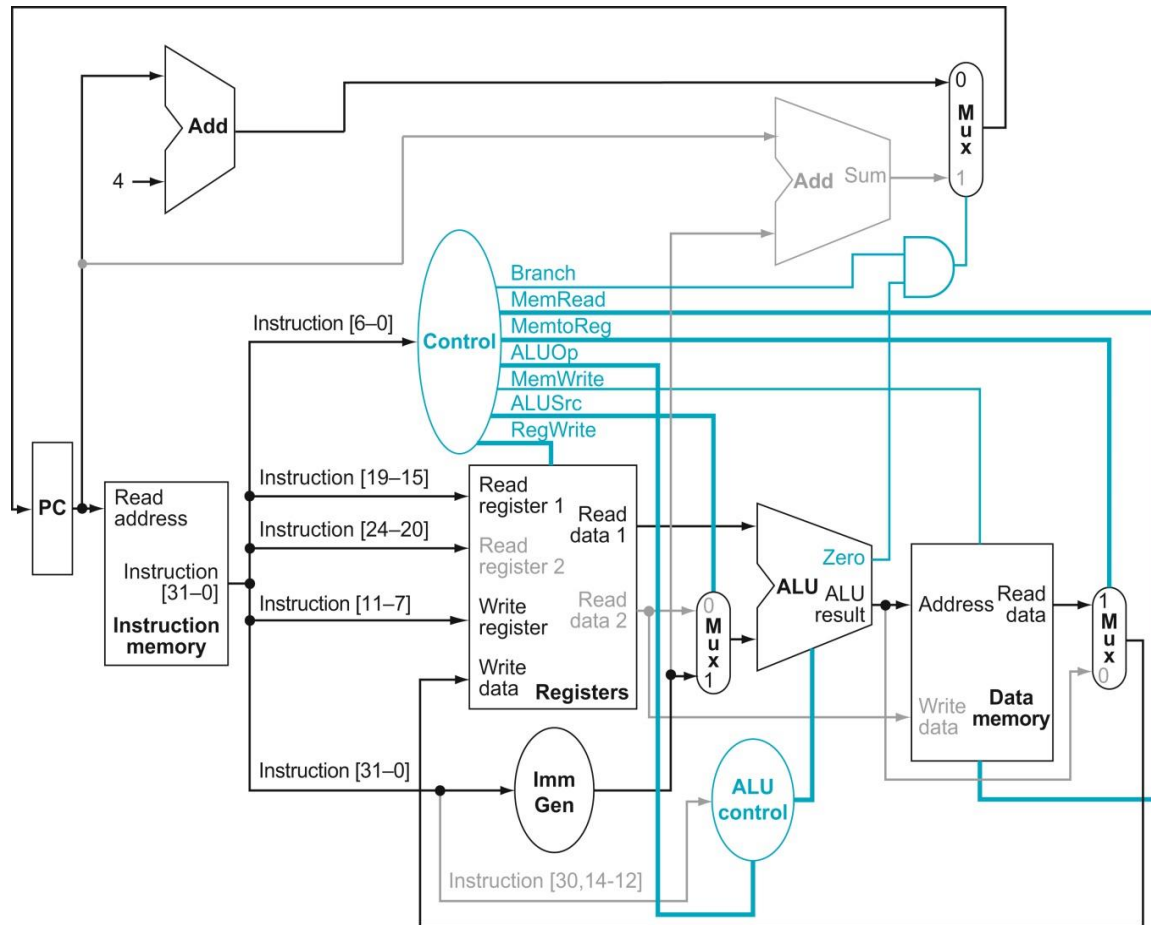


	lw	sw
RegWrite	1	0
ALUSrc	1	1
Branch	0	0
MemtoReg	1	X
MemRead	1	0
MemWrite	0	1
ALUOp1	0	0
ALUOp0	0	0

# Control for Branch on Equal

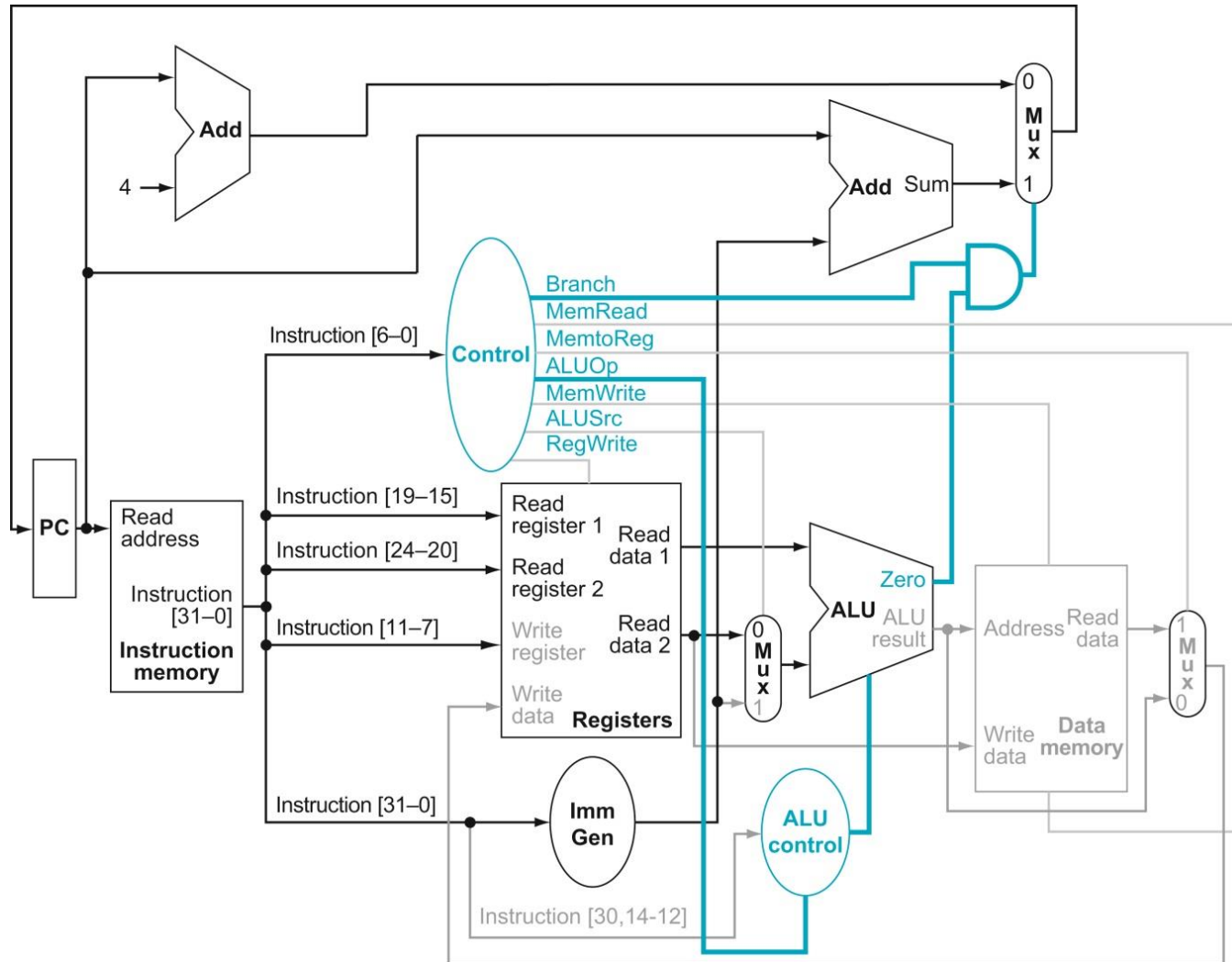

RegWrite	0
ALUSrc	0
Branch	1
MemtoReg	X
MemRead	0
MemWrite	0
ALUOp1	0
ALUOp0	1

# Single-Cycle Data Path with Control

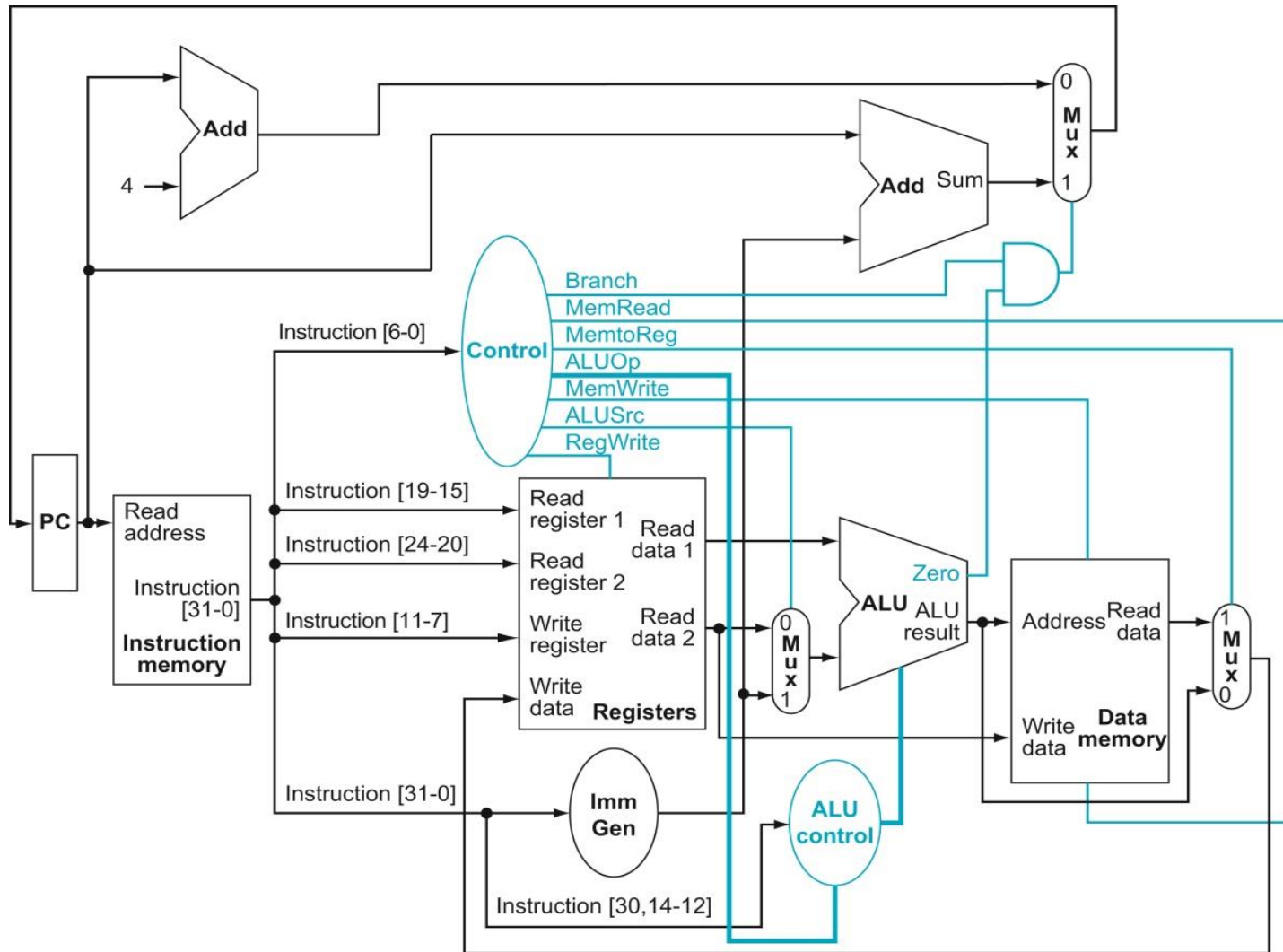

# ***Design of the ALU Control Unit***

---

- **ALU used for R-type**
  - Function depends on funct field

<b>ALU control</b>	<b>Function</b>
0000	AND
0001	OR
0010	add
0110	subtract

# ALU Control for R-Type

## • 2-bit ALUOp derived from opcode

- Combinational logic derives ALU control
- Think of the table as IF statements
  - If opcode says it's R-type, then set ALUOp=10
  - If ALUOp=10, then tell ALU Control to use funct3 and funct7 to set ALU Control

opcode	ALUOp	Operation	funct7	funct3	ALU function	ALU control
R-type	10	add	0000000	000	add	0010
		subtract	0100000	000	subtract	0110
		AND	0000000	111	AND	0000
		OR	0000000	110	OR	0001



# ALU Control for lw/sw

- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control
- ALU used for Load/Store: F = add

opcode	ALUOp	Operation	funct7	funct3	ALU function	ALU control
lw	00	load word	XXXXXXXX	XXX	add	0010
sw	00	store word	XXXXXXXX	XXX	add	0010
R-type	10	add	0000000	000	add	0010
		subtract	0100000	000	subtract	0110
		AND	0000000	111	AND	0000
		OR	0000000	110	OR	0001


# ALU Control for beq

---


- beq F = sub
- lw/sw F = add
- R-type F depends on funct3/funct7

opcode	ALUOp	Operation	funct7	funct3	ALU function	ALU control
beq	01	branch on equal	XXXXXXXX	XXX	sub	0110
lw	00	load word	XXXXXXXX	XXX	add	0010
sw	00	store word	XXXXXXXX	XXX	add	0010
R-type	10	add	0000000	000	add	0010
		subtract	0100000	000	subtract	0110
		AND	0000000	111	AND	0000
		OR	0000000	110	OR	0001

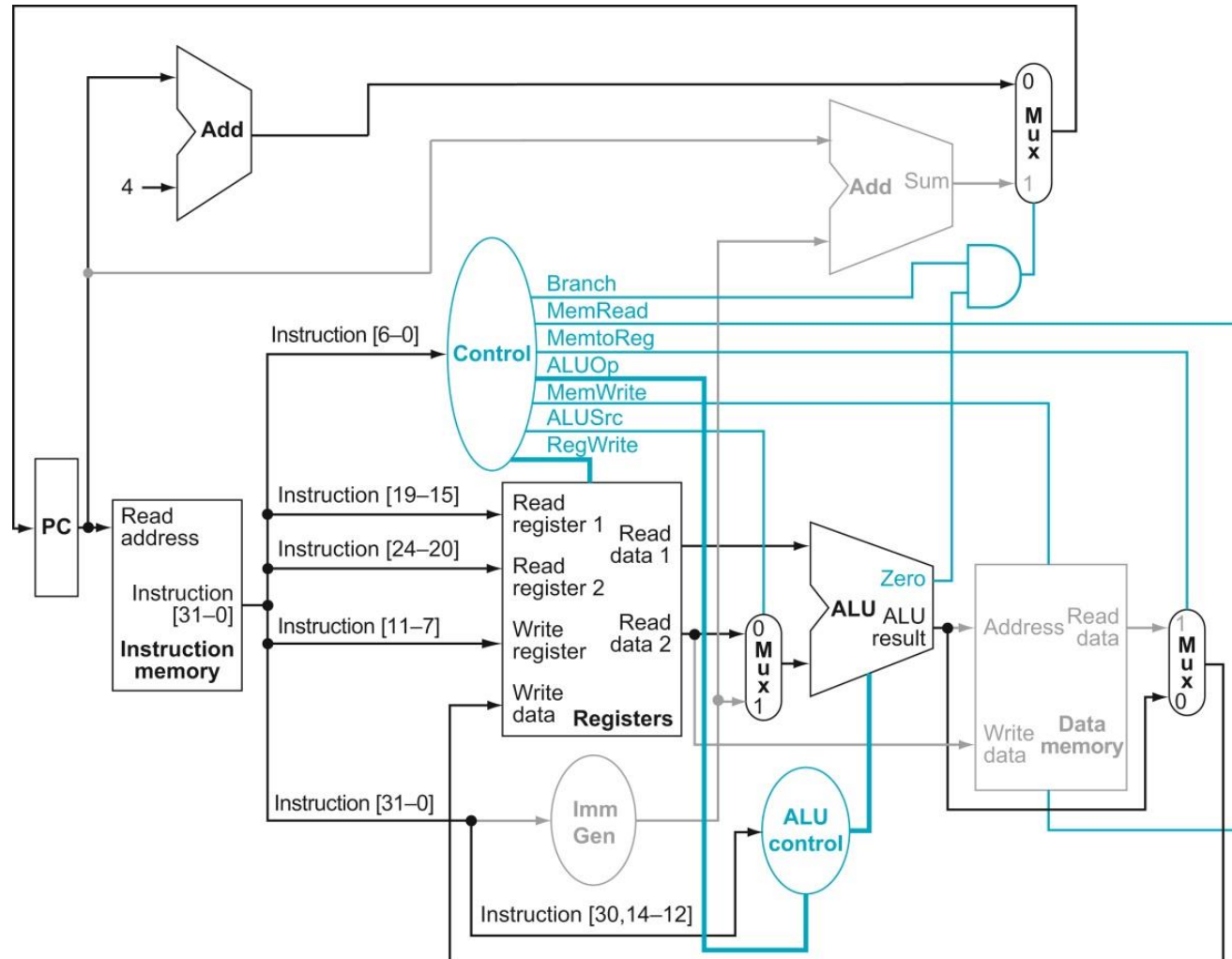
# The Datapath in Operation for R-type Instructions (e.g. `add t1, t2, t3`)




# *The Datapath in Operation for 1w*

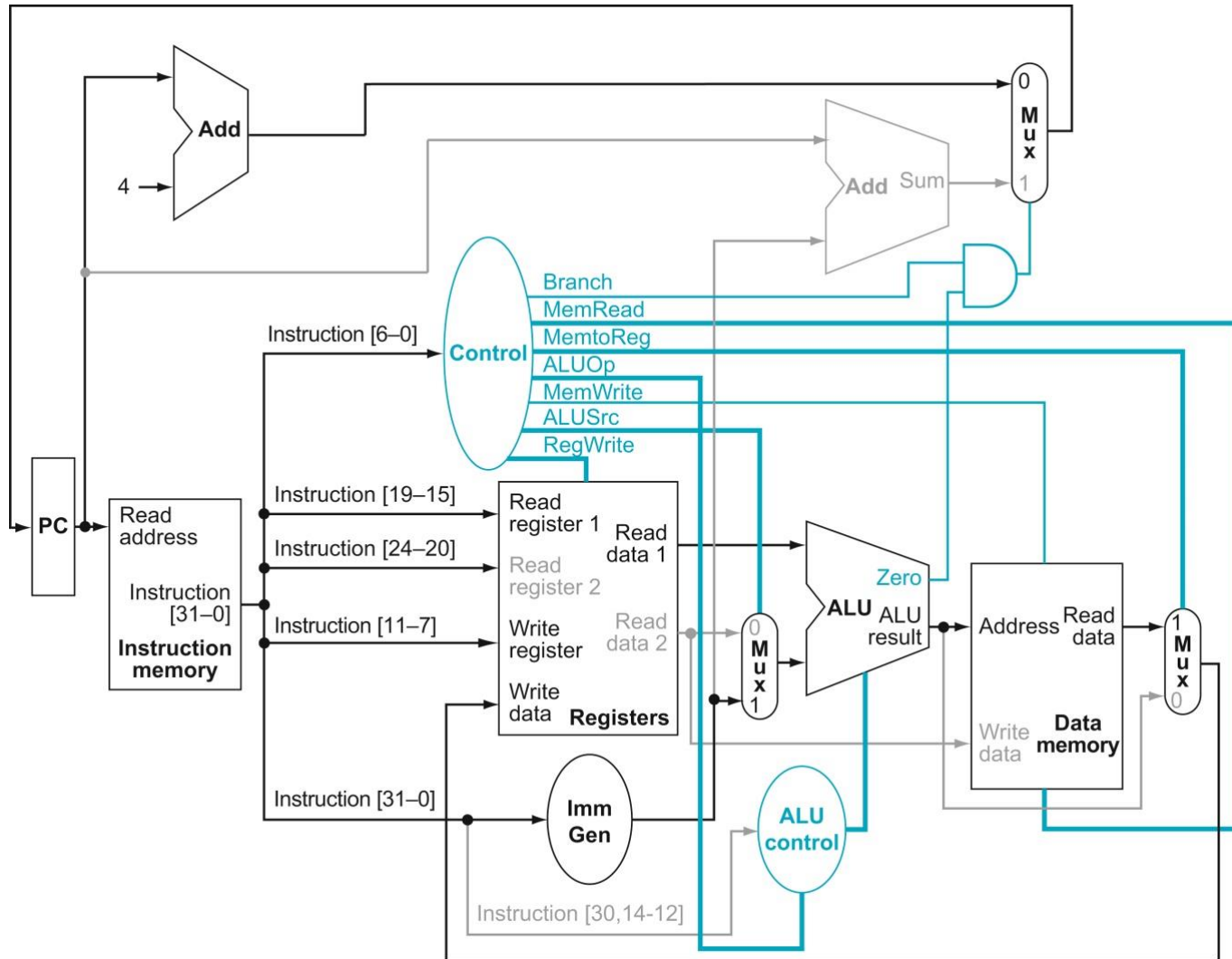


# *The Datapath in Operation for beq*

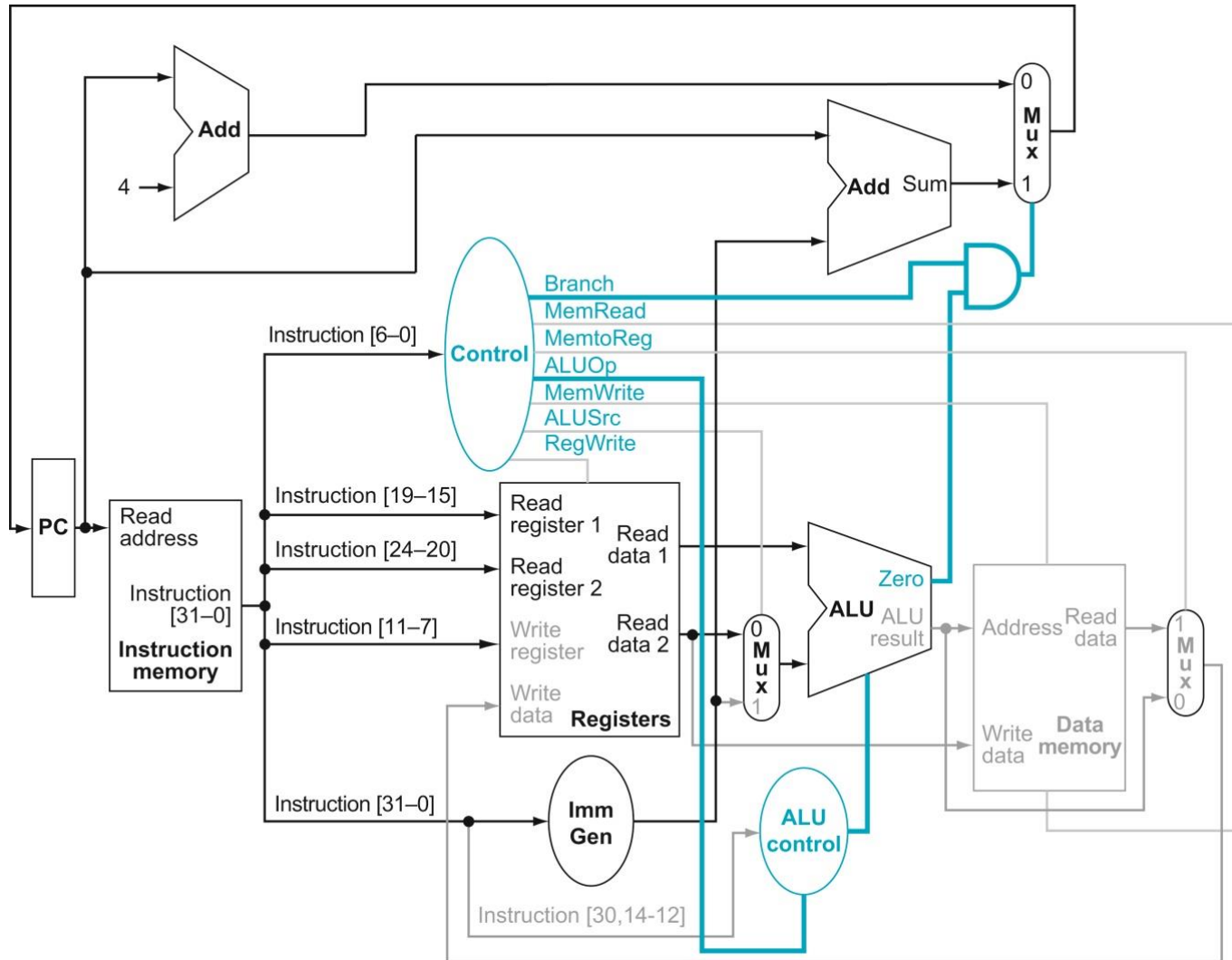

# Problem: 1w t1, 32 (t2)

 

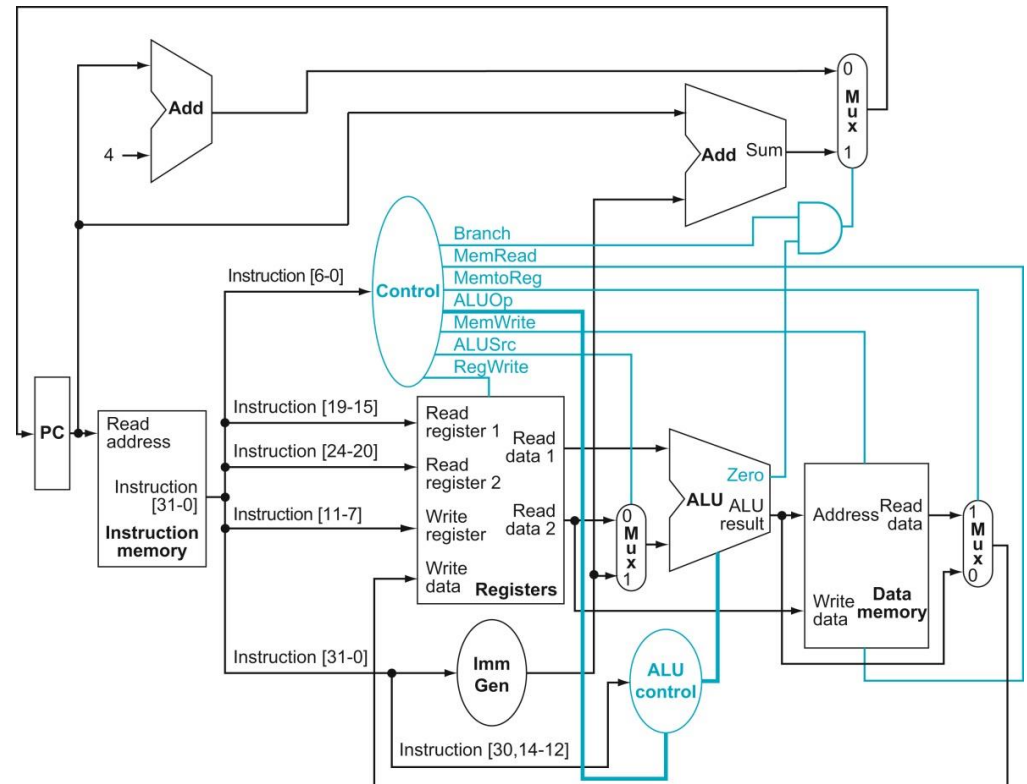- Inactive blocks:
- Instruction [19-15]=
- Instruction [24-20] =
- Instruction [11-7]=
- Branch=
- MemRead=
- MemtoReg=
- ALUOp= 00
- MemWrite=
- ALUSrc=
- RegWrite=



# *More Questions*

---

- What is routed to 'Write register'?
- What value comes out of ImmGen?
- Why does it not matter what value goes to Read register 2?
- Why does it not matter if the Zero flag is set or not coming out of the ALU?
- What other inputs are ignored due to control signals?

# Summary of Single-Cycle Datapath

---

## • 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that affects the register transfer
- 5. Assemble the control logic

## • RISC-V makes it easier

- Instructions same size
- Source registers always in same place
- Immediates minimize placement differences
- Operations always on registers/immediates

## • Single cycle datapath => CPI=1, CCT = long