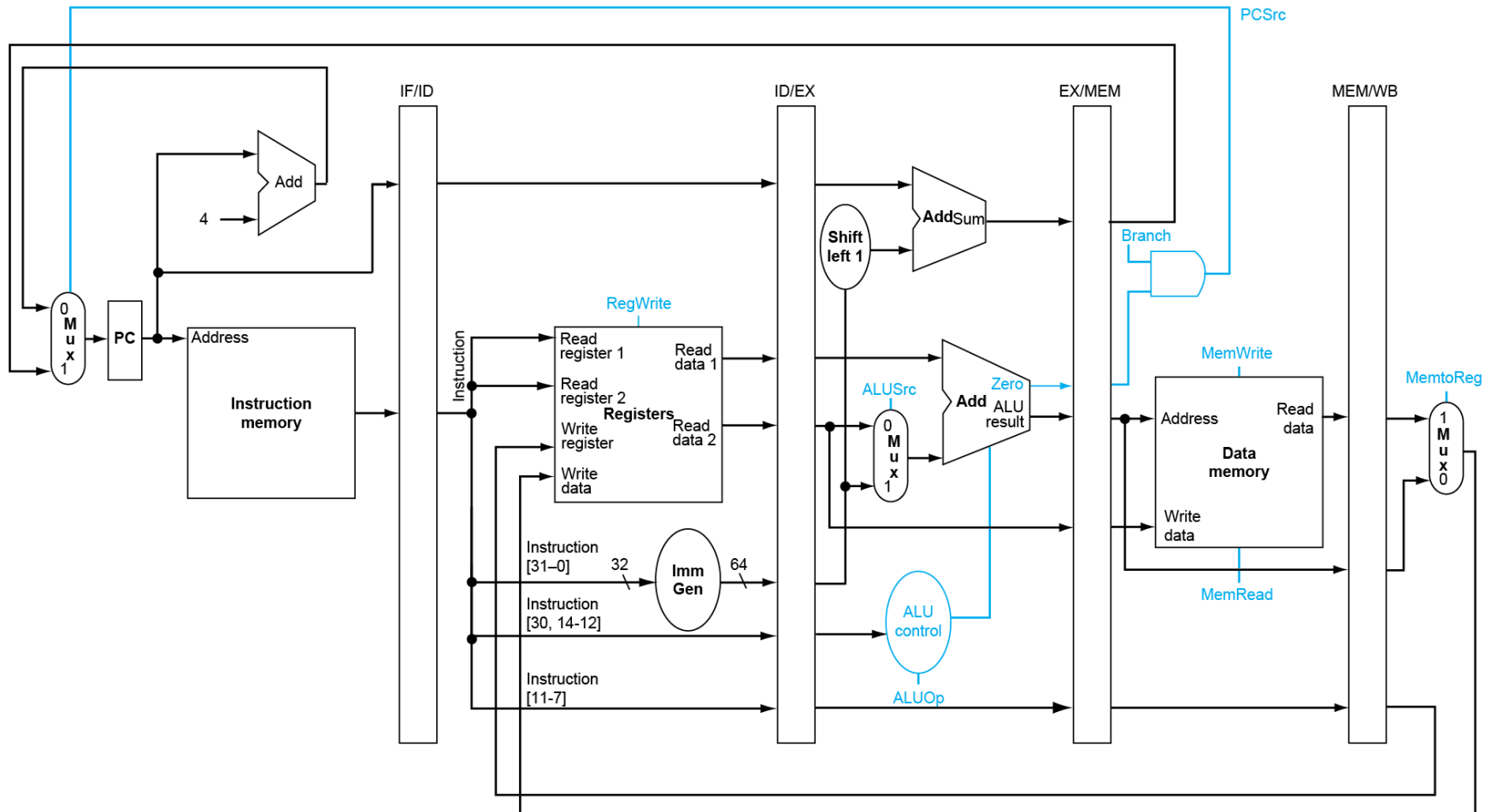


Pipelined Datapath Control



Observations

- **No write control for all pipeline registers and PC**
 - they are updated at every clock cycle.
- **To specify the control for the pipeline**
 - set the control values during each pipeline stage.
- **Control lines can be divided into 5 groups:**
 - IF — NONE
 - ID — NONE
 - EXE — ALUOp, ALUSrc
 - MEM — Branch, MemRead, MemWrite
 - WB — MemtoReg, RegWrite


Control for Pipelined Datapath

Instruction	Execution/address calculation stage control lines		Memory access stage control lines			Write-back stage control lines	
	ALUOp	ALUSrc	Branch	Mem-Read	Mem-Write	Reg-Write	Memto-Reg
R-format	10	0	0	0	0	1	0
lw	00	1	0	1	0	1	1
sw	00	1	0	0	1	0	X
beq	01	0	1	0	0	0	X


- Control signals are generated at ID stage, how to pass them to other stages?

Pass Control Signals

 - Extend the pipeline registers to include control information



The Complete Pipelined Datapath

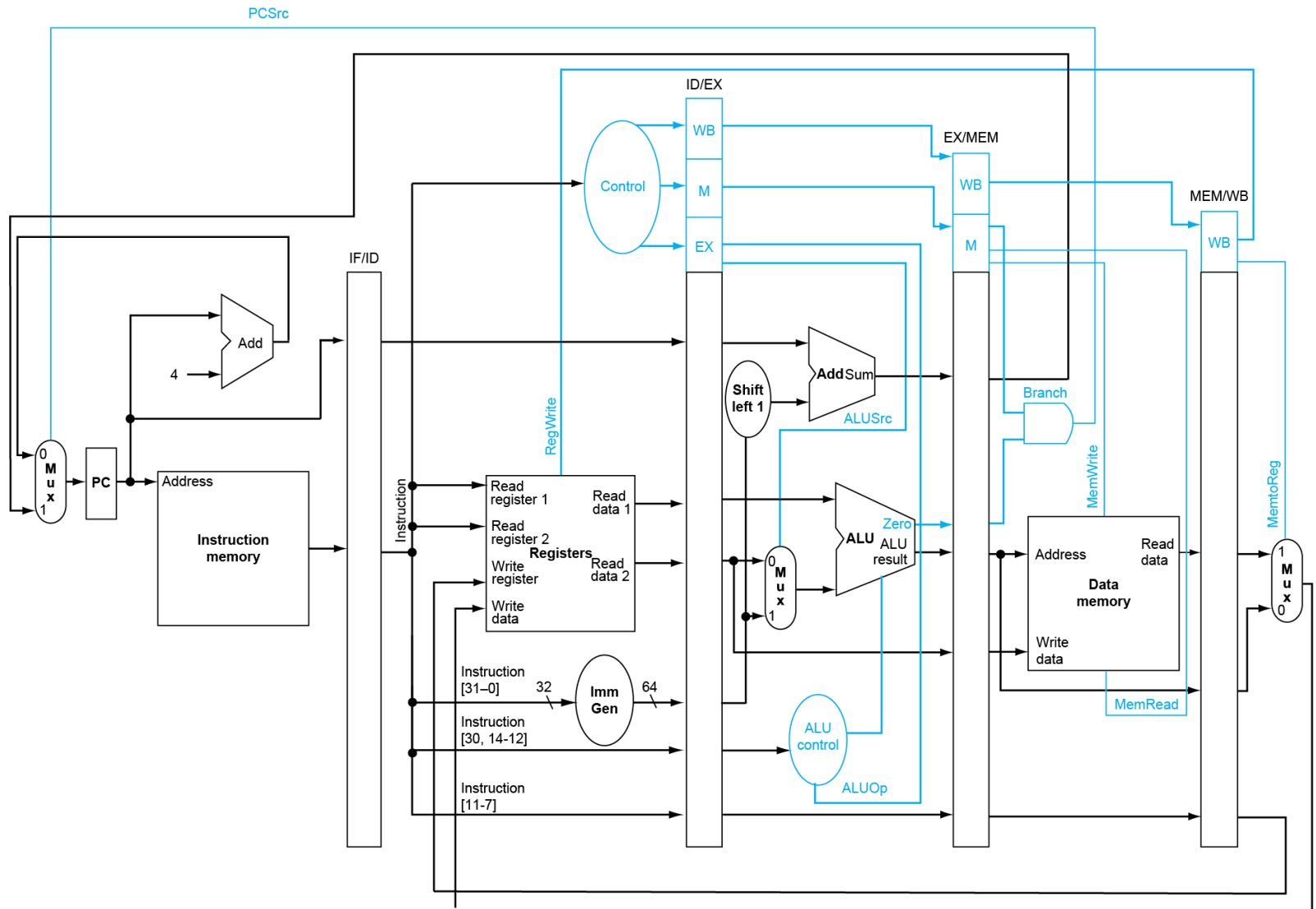


Example Pipeline Execution

**Note our instructions are independent of each other
(no data hazards)**


```
lw    x10, 40(x1)  
sub    x11, x2, x3  
and    x12, x4, x5  
or     x13, x6, x7  
add    x14, x8, x9
```




Clock Cycle 2

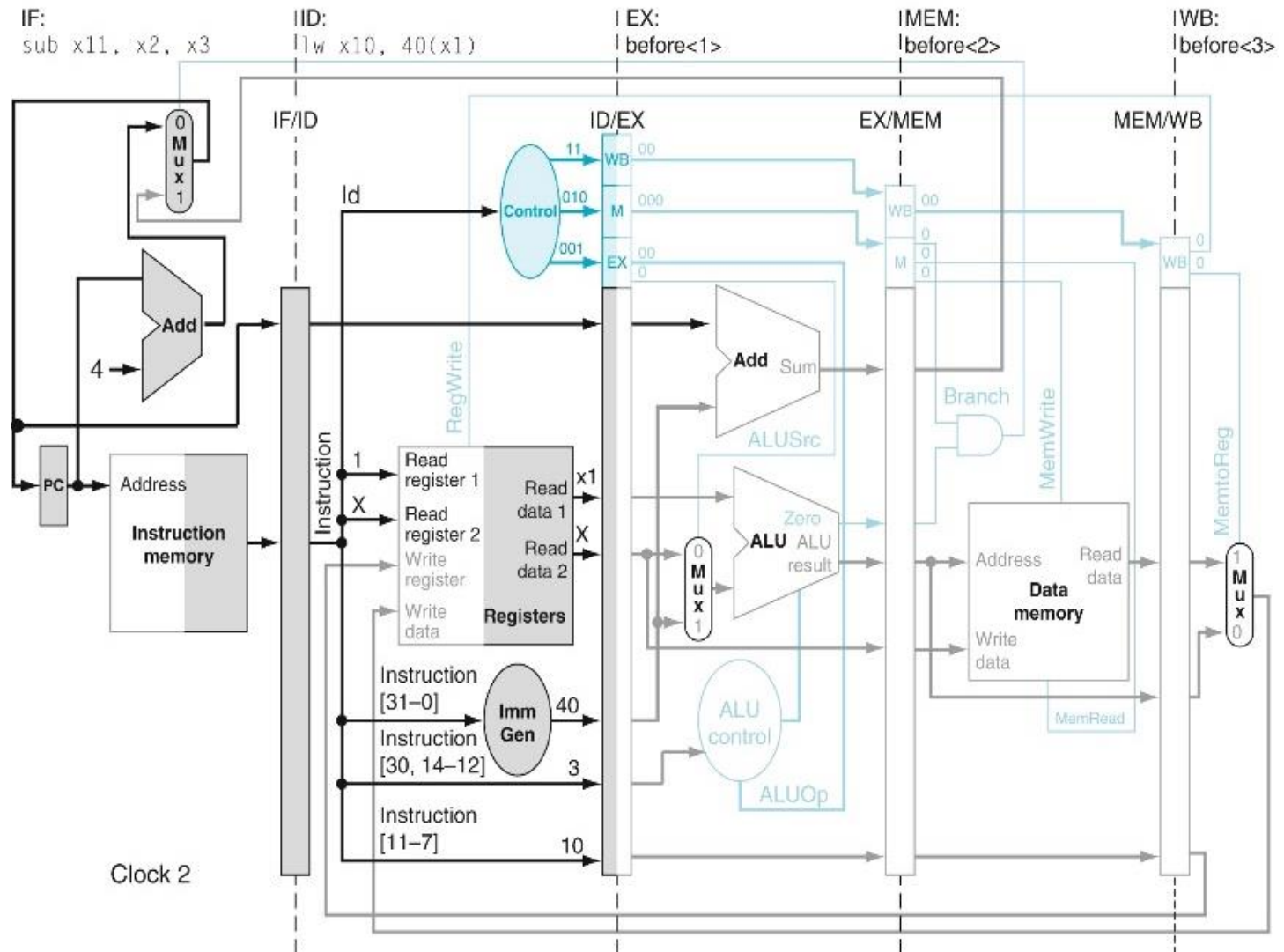


Clock Cycle 3

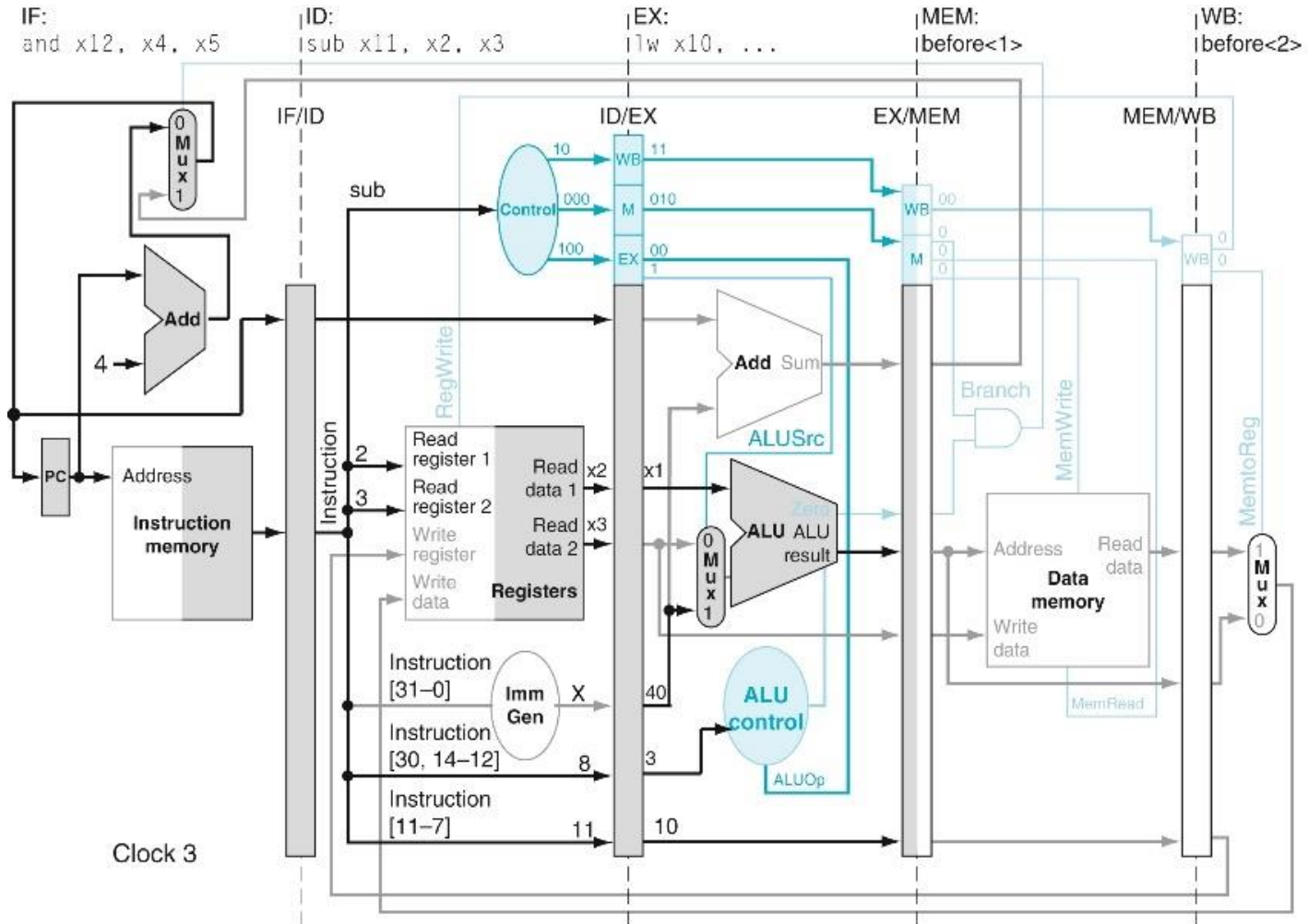


Clock Cycle 4

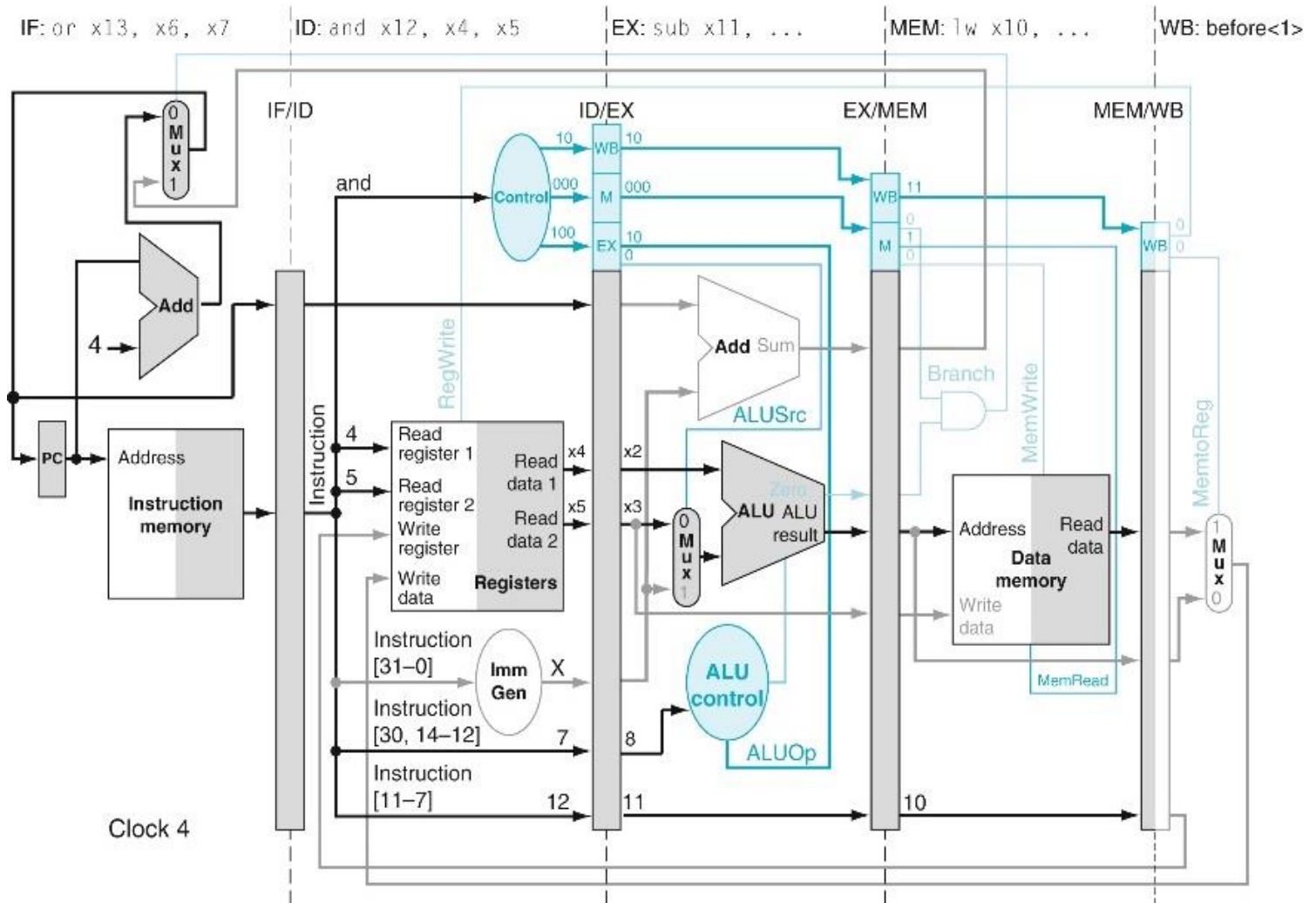

Clock Cycle 6

 

Clock Cycle 7

 

Clock Cycle 9

